

ADC / DAC

ECET 209 – Introduction to
Microcontrollers

Overview

- Review Analog and Digital Converters
- Preview Lab #9
- Do a Group Activity

Digital vs. Analog

- Most values are analog in nature
 - Temperature
 - Speed
 - Position
 - Etc
- Digital systems are used to process information


Digital vs. Analog

- Digital systems are used to process info
 - Somehow need to convert an analog value into a digital value
 - Perform digital operations on the data
 - Somehow need to convert the digital results back into an analog quantity

Digital vs. Analog

- Digital systems are used to process info
- A couple Major Examples
 - CD's
 - MP3's
 - DVD's

Digital vs. Analog

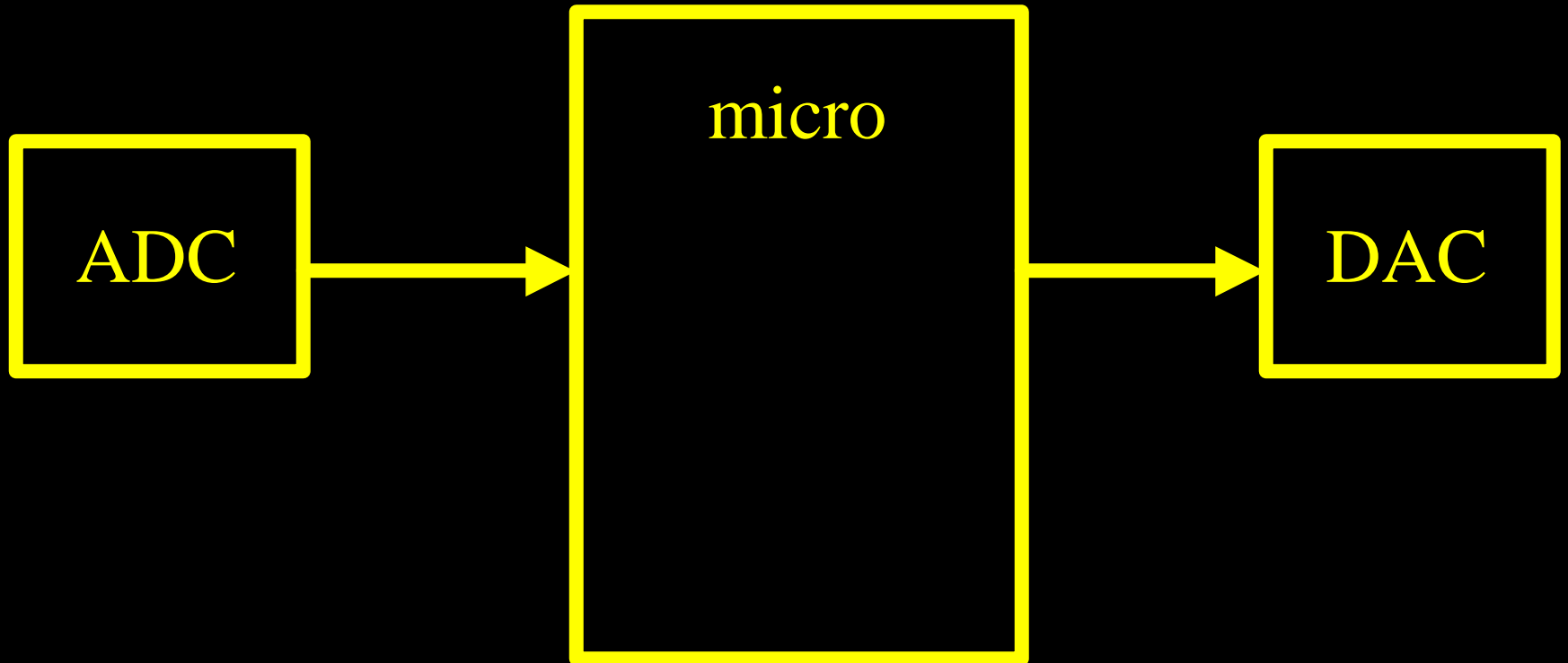

ADC & DAC

- ADC – Analog to Digital Converter
- DAC – Digital to Analog Converter
- ADC and DAC operations are required at the input and output from a digital processing system that deals with analog quantities.

Digital Displays

- Digital displays are easier to read (by consumers)
- Accuracy of digital displays depends on the accuracy of the A/D conversion

Analog/Digital Characteristics

- Performance Criteria
 - Resolution
 - Sampling Rate
 - Speed
 - Linearity

Analog Interface Module

- Lab Hardware board for Analog applications
 - 8-bit Digital to Analog converter (AD558)
 - 10-bit Analog to Digital converter (AD573)
 - 0 to 10 volts
 - Pot to adjust the input analog voltage
 - Analog meter to display the analog input or output
 - Selector switches for input and the meter

Digital to Analog Converter

- Takes 8-bit value and converts it to an analog voltage
- A digital value of 0x00 yields 0 volts out
- A digital value of 0xFF yields 10 volts out

Digital to Analog Converter

- Takes 8-bit value and converts it to an analog voltage
- A digital value of 0x00 yields 0 volts out
- A digital value of 0xFF yields 10 volts out

$$\text{resolution} = V_{\text{out_max}} / 2^8 - 1$$

Digital to Analog Converter

- Takes 8-bit value and converts it to an analog voltage
- A digital value of 0x00 yields 0 volts out
- A digital value of 0xFF yields 10 volts out

$$\text{resolution} = V_{\text{out_max}} / 2^8 - 1$$

$$\text{resolution} = 10 \text{ volts} / 255$$

Digital to Analog Converter

- Takes 8-bit value and converts it to an analog voltage
- A digital value of 0x00 yields 0 volts out
- A digital value of 0xFF yields 10 volts out

$$\text{resolution} = V_{\text{out_max}} / 2^8 - 1$$

$$0.0392157 = 10 \text{ volts} / 255$$

Digital to Analog Converter

- Takes 8-bit value and converts it to an analog voltage
- A digital value of 0x00 yields 0 volts out
- A digital value of 0xFF yields 10 volts out

$$\text{resolution} = V_{\text{out_max}} / 2^8 - 1$$

$$0.0392157 = 10 \text{ volts} / 255$$

$$V_{\text{out}} = \text{resolution} * \text{digital input}$$

Analog to Digital Converter

- Takes an analog voltage and converts it to a digital value
- The AD573 is a 10-bit converter
- An analog value of 0 volts will produce a digital output of 0x000
- An analog value of 10 volts will produce a digital output of 0x3FF

Analog to Digital Converter

- Resolution of the ADC is:

$$\text{resolution} = V_{\text{in_max}} / 2^{10} - 1$$

$$\text{resolution} = 10 / 1023$$

$$0.009775 = 10 / 1023$$

or approximately

10mV per bit when using 10-bits of accuracy

Analog to Digital Converter

- Resolution is a function of the number of data bits in the result
- What if we only wanted 8-bits of data?

Analog to Digital Converter

- Resolution of the ADC is:

$$\text{resolution} = V_{\text{in_max}} / 2^8 - 1$$

$$\text{resolution} = 10 / 255$$

$$0.03921 = 10 / 255$$

or approximately

40mV per bit when using 8-bits of accuracy

8-bits vs. 10-bits

- The number of data bits is determined by the resolution requirements of the application
- The resolution has a direct impact on the accuracy of the system

10mV or 40mV


8-bits vs. 10-bits

- A system with 10-bits of data vs. a system with only 8-bits of data is 4 times more resolution.
- Remember, 2^{power}
- In this case, the power is 2 and therefore the difference is a factor of 4.


Using the ADC

- *Most* ADC's require some type of “kick” to start the next conversion
- A *flag* will indicate the state or status of the current conversion
- The new data can be read only when the conversion has been completed


Timing Diagram for ADC

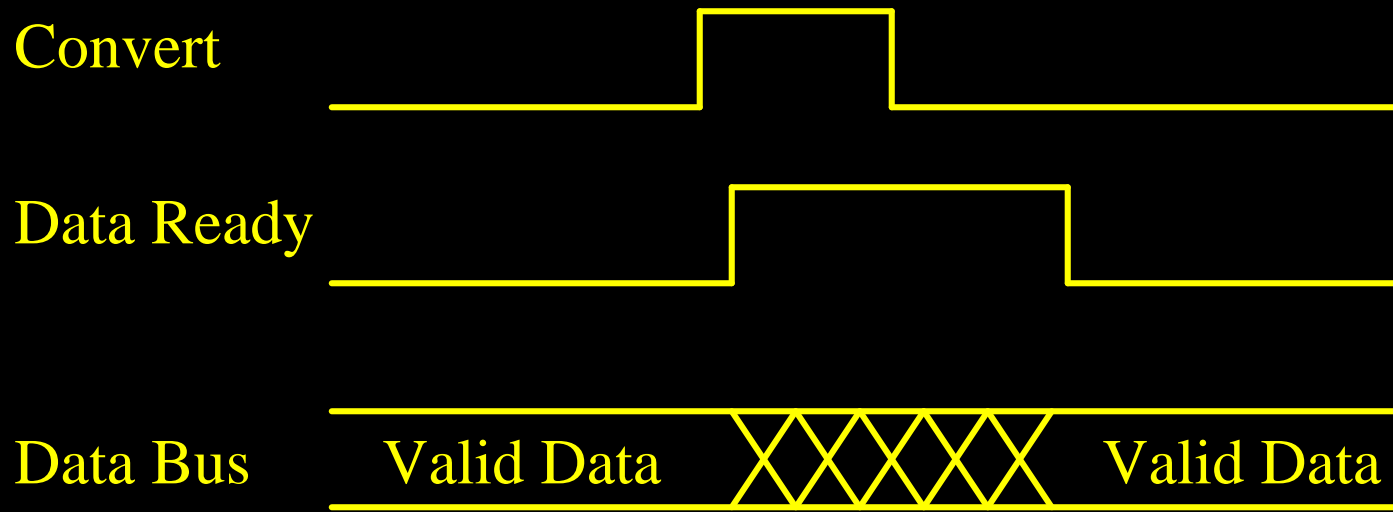


Timing Diagram for ADC

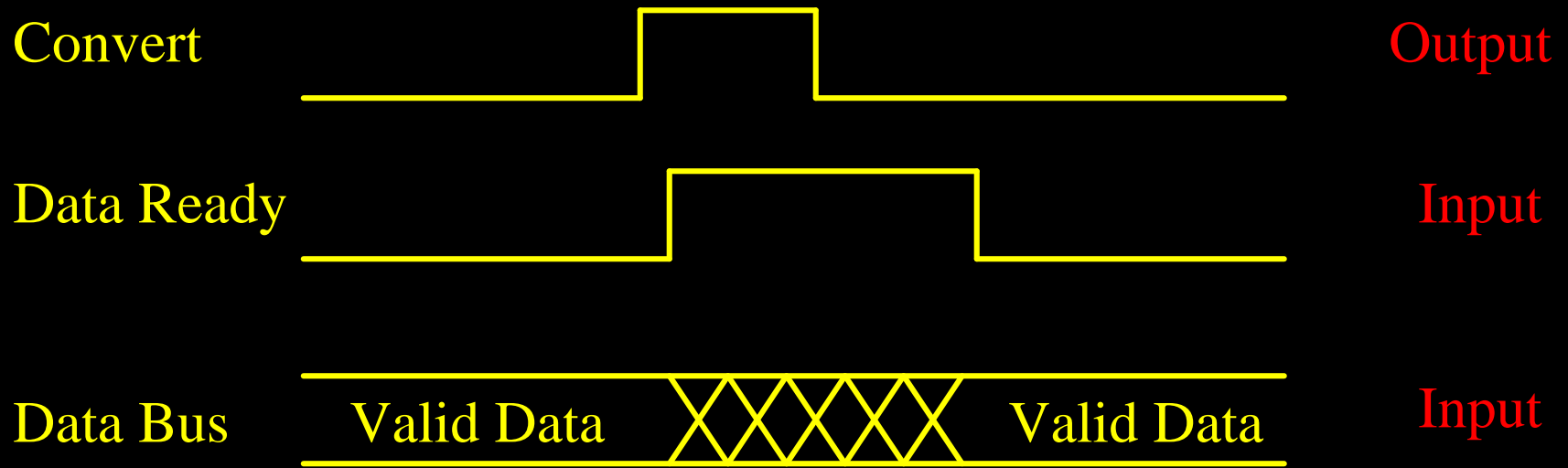


Timing Diagram for ADC

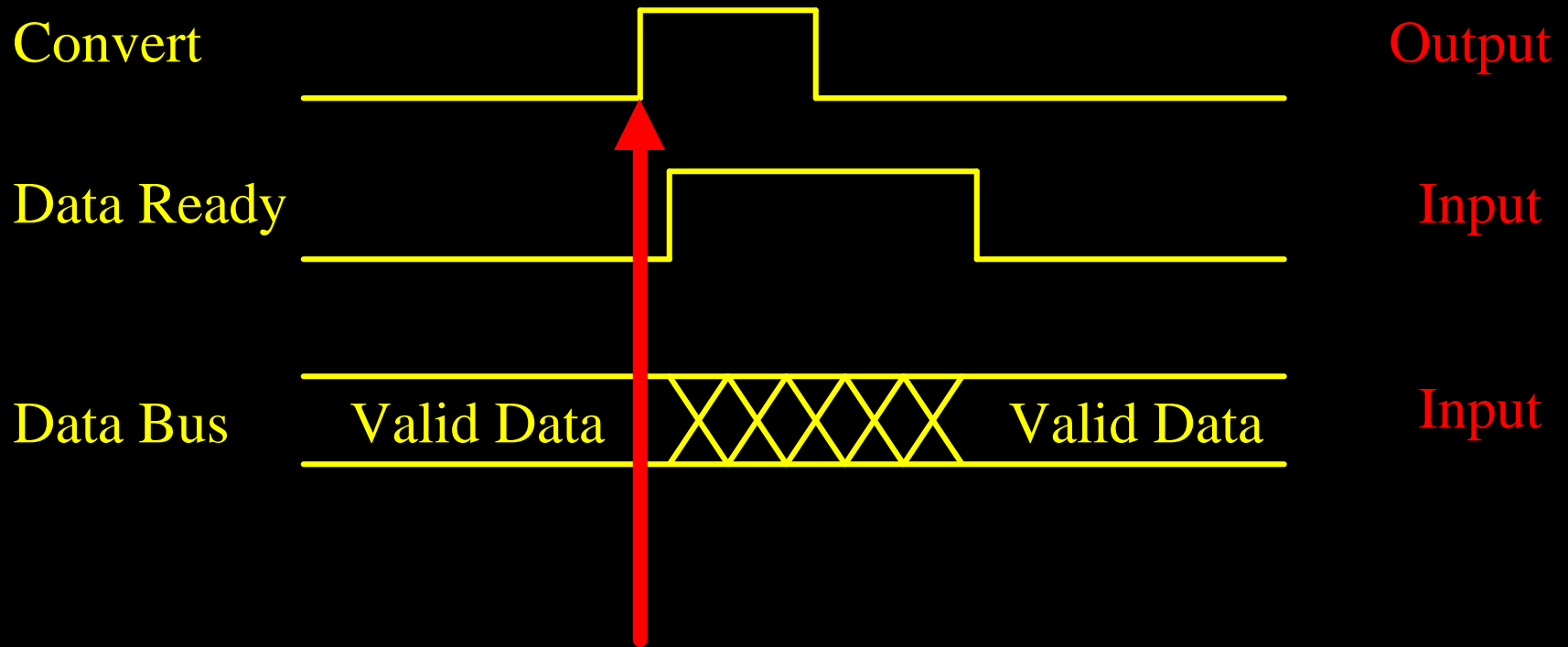


Timing Diagram for ADC

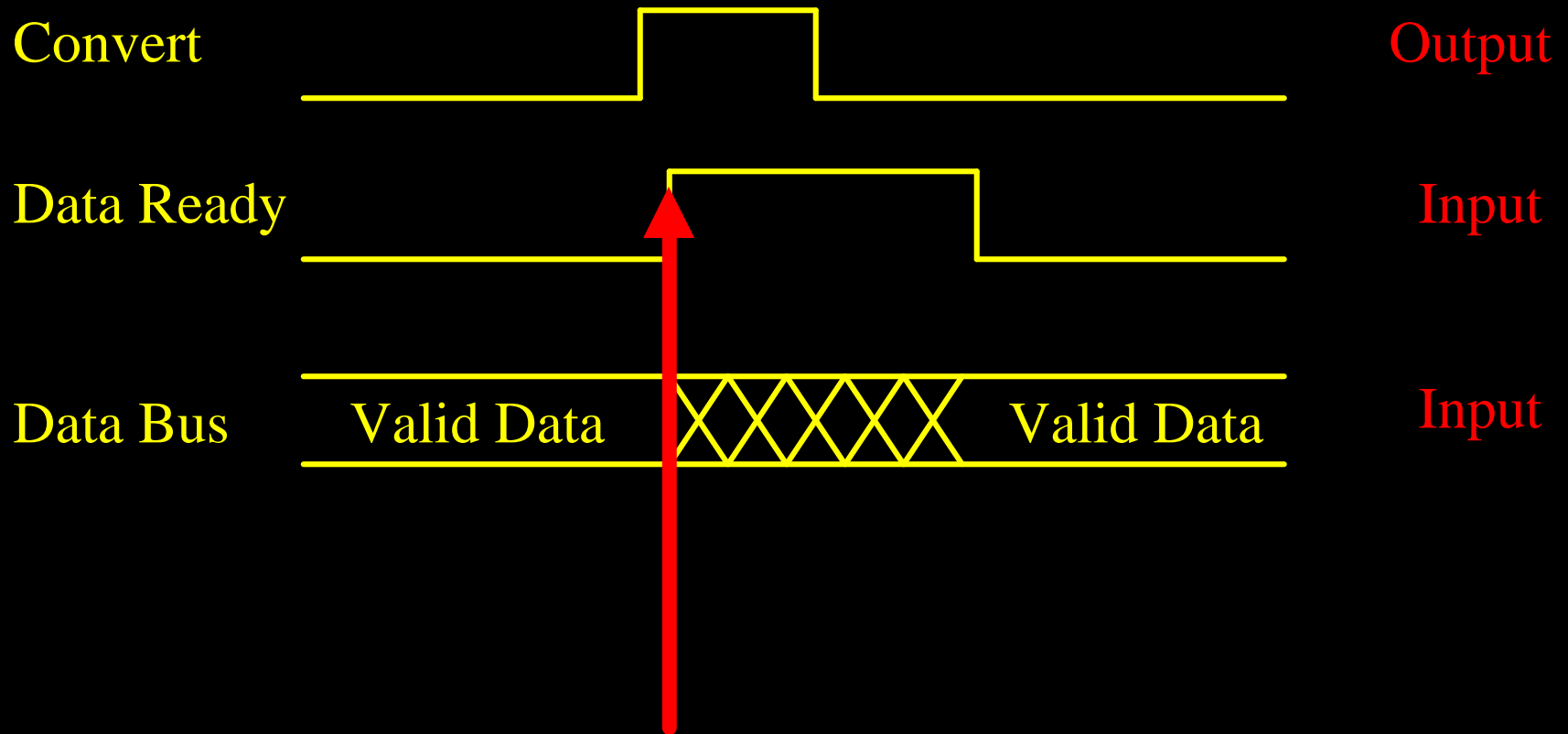


Timing Diagram for ADC

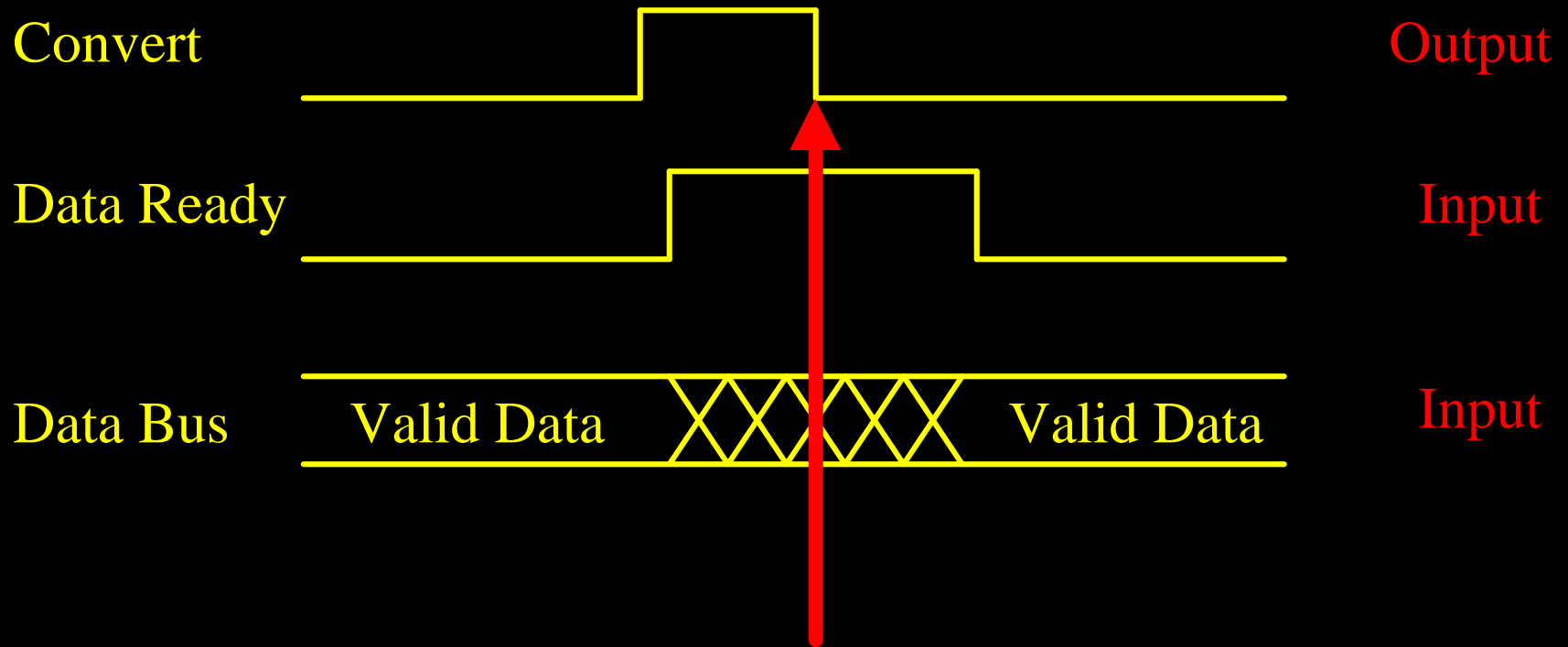

Timing Diagram for ADC

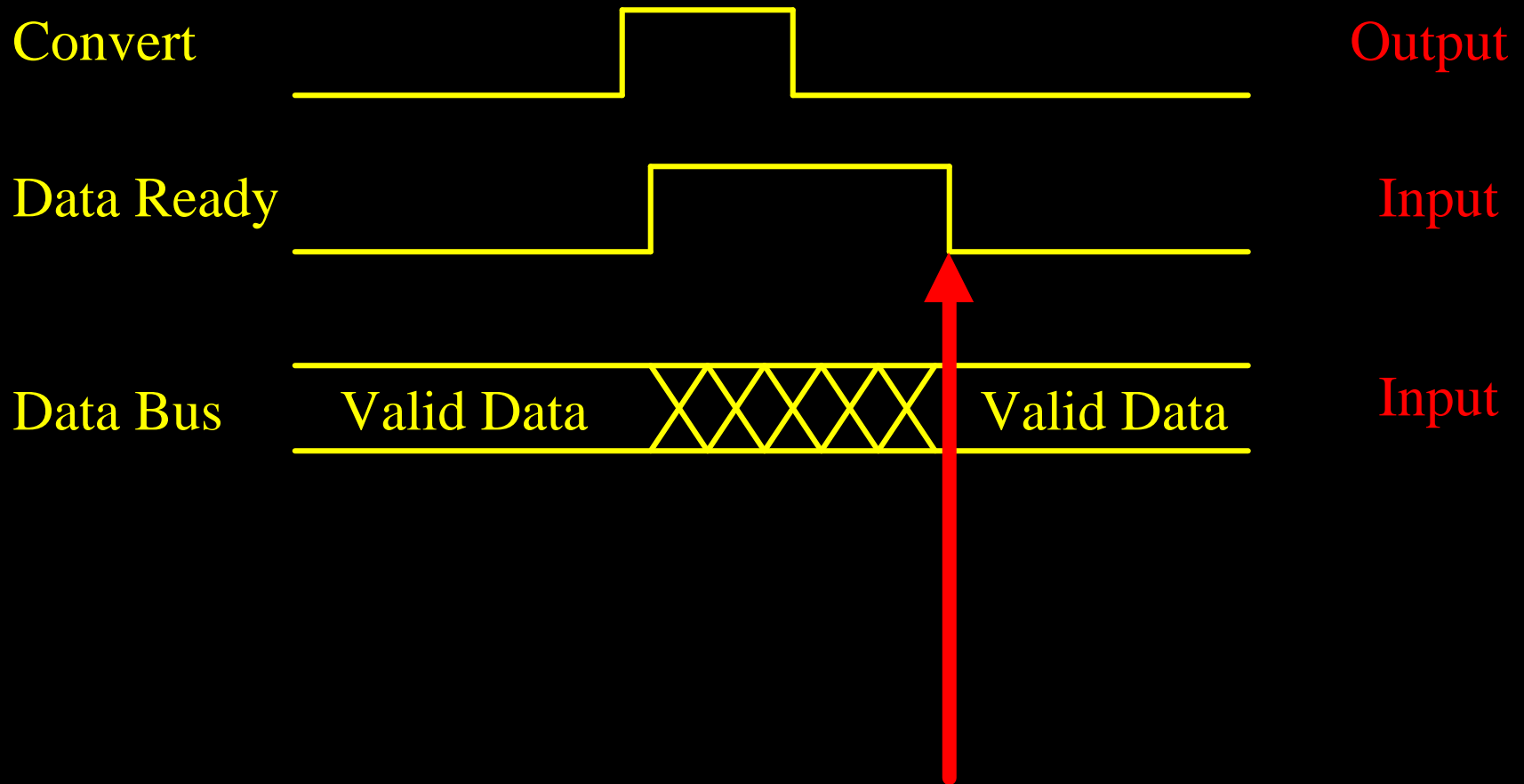


Timing Diagram for ADC

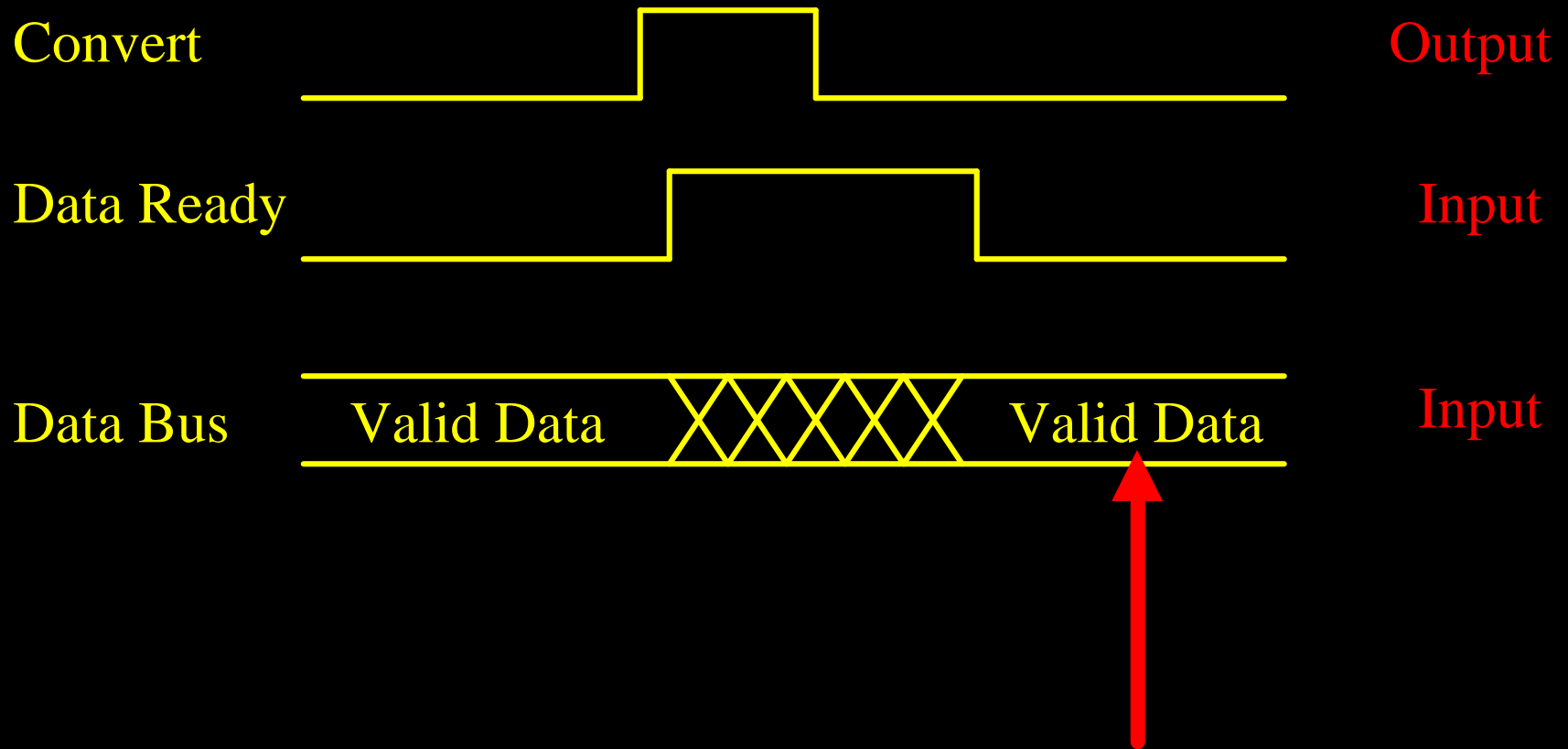


Solution Steps to use the ADC

1. Set the convert line high
2. Wait for Data Ready to go high
3. Clear the convert line
4. Wait for the Ready Line to go low
5. Read the result of the conversion


Analog and Digital Converters

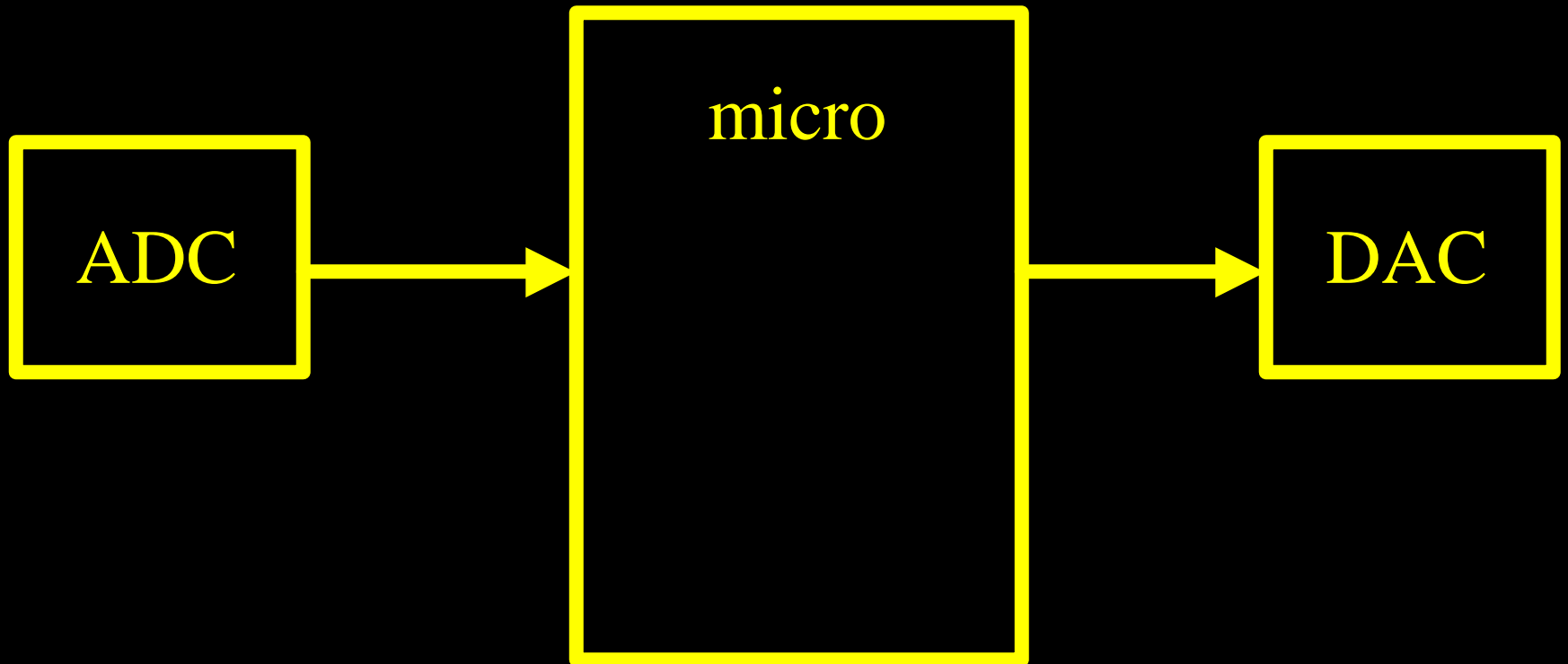


Digital to Analog Converter

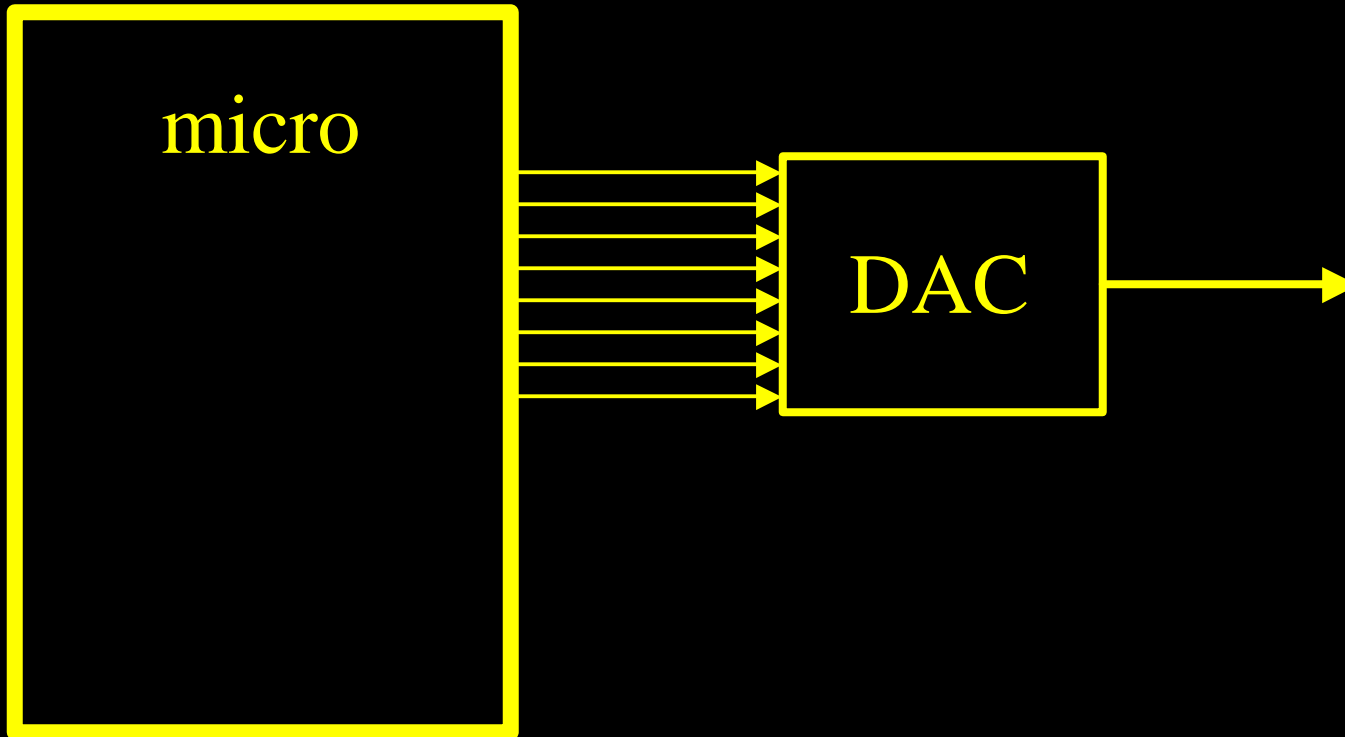


Digital to Analog Converter

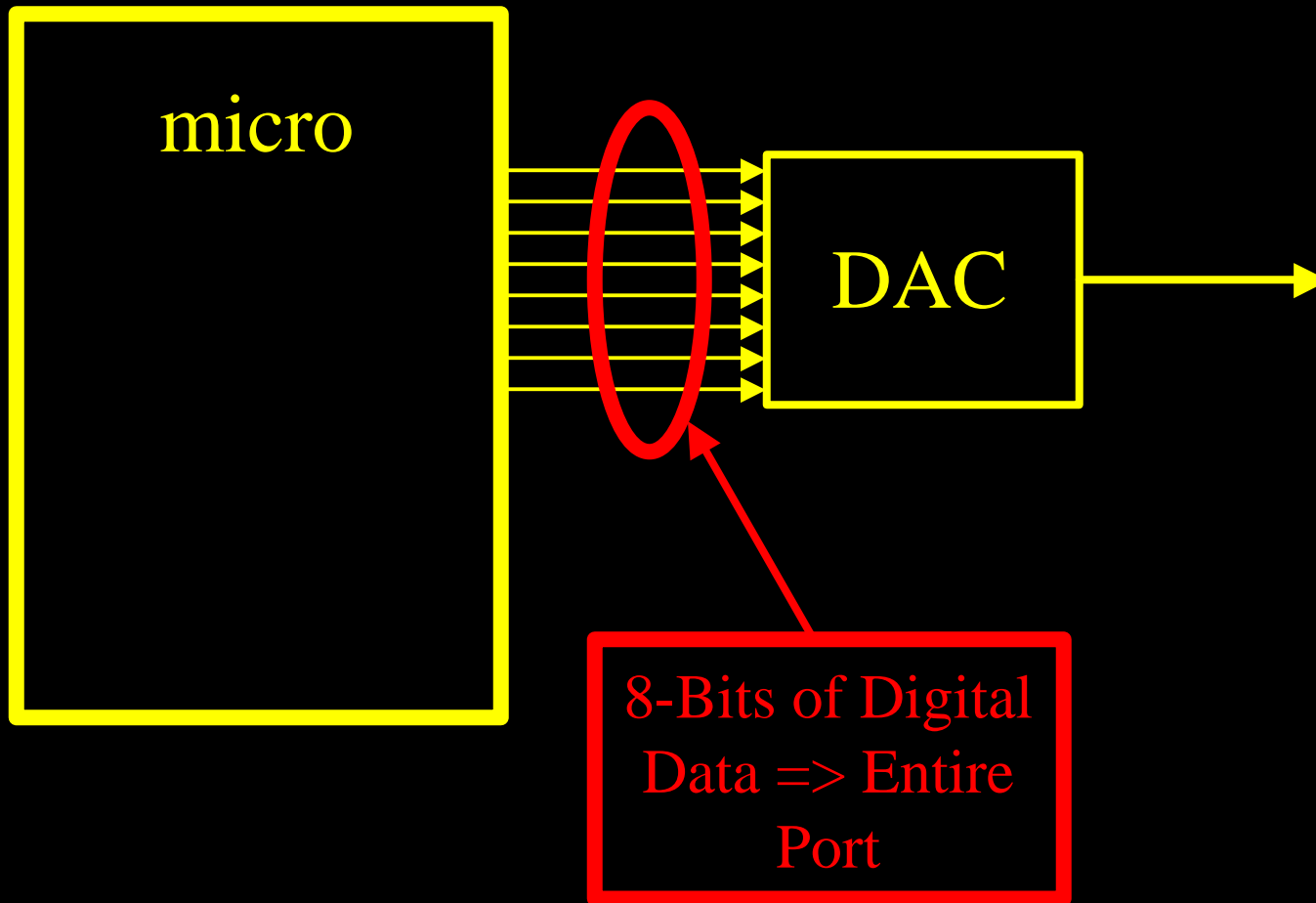

Digital to Analog Converter

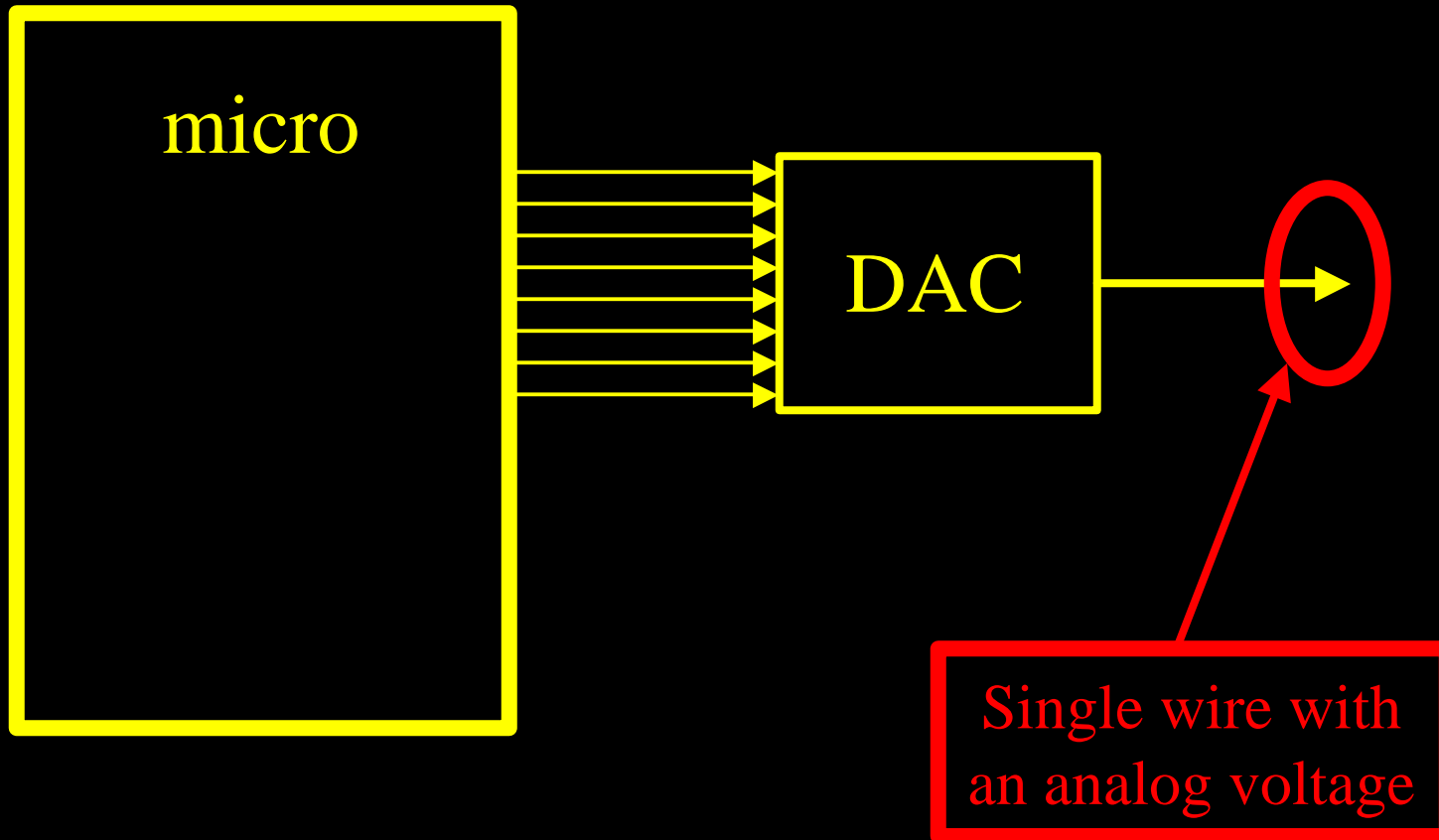


Digital to Analog Converter

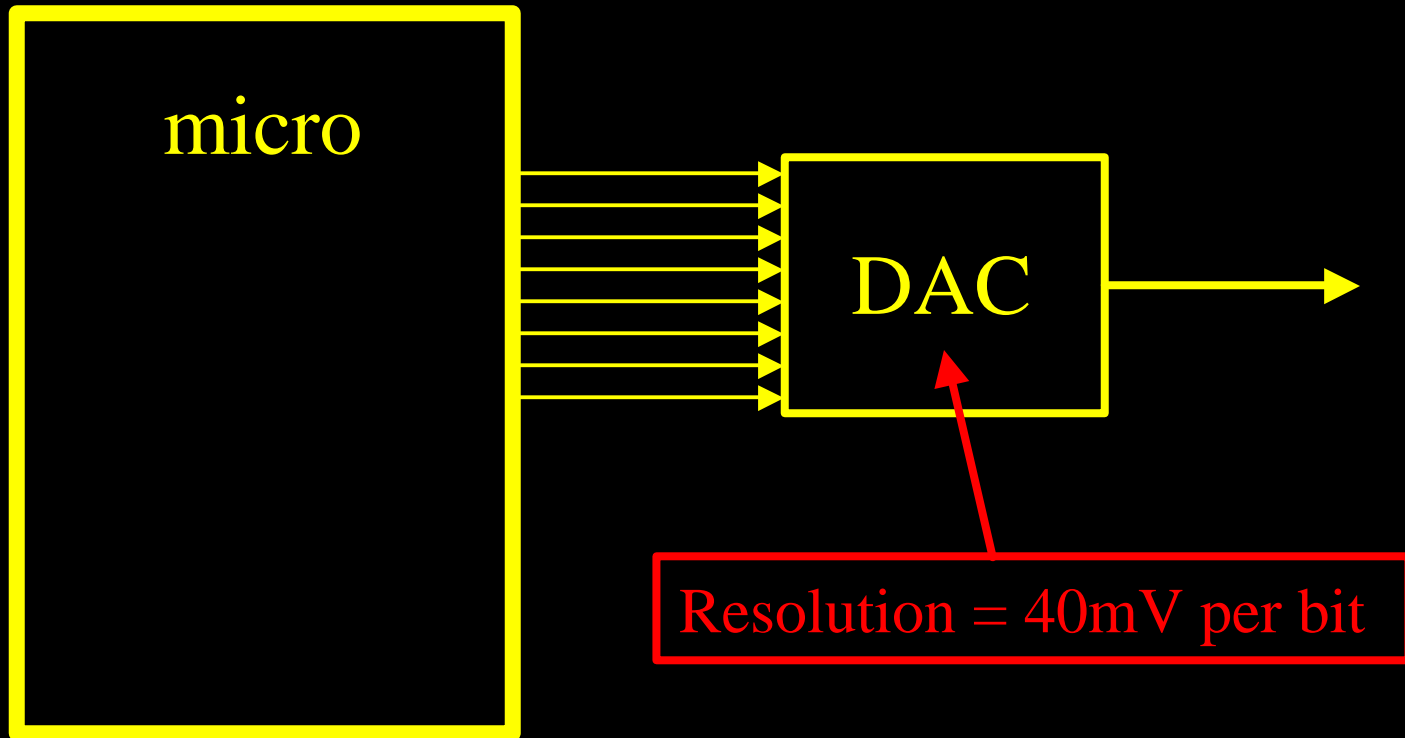


$$\text{resolution} = V_{\text{out_max}} / 2^8 - 1$$


Digital to Analog Converter

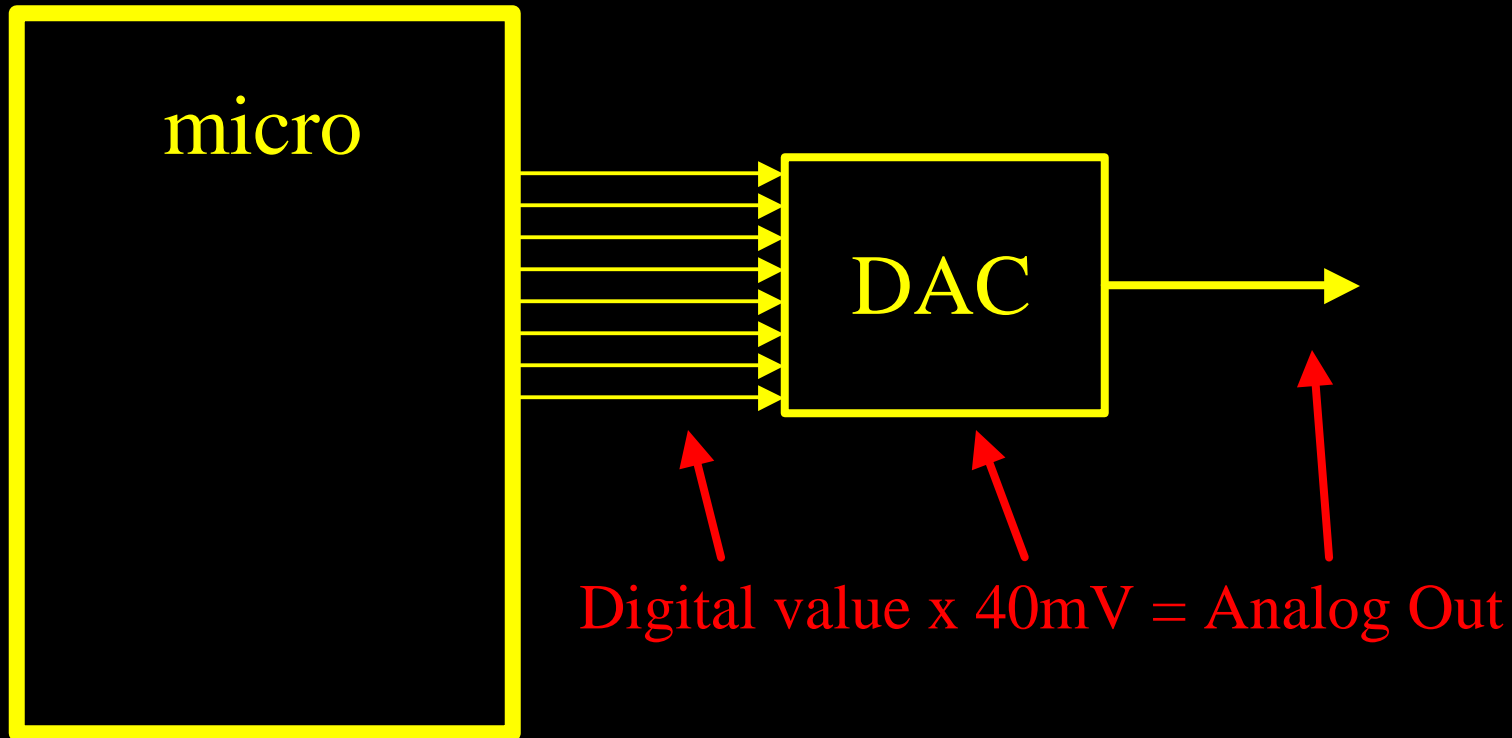


Digital to Analog Converter

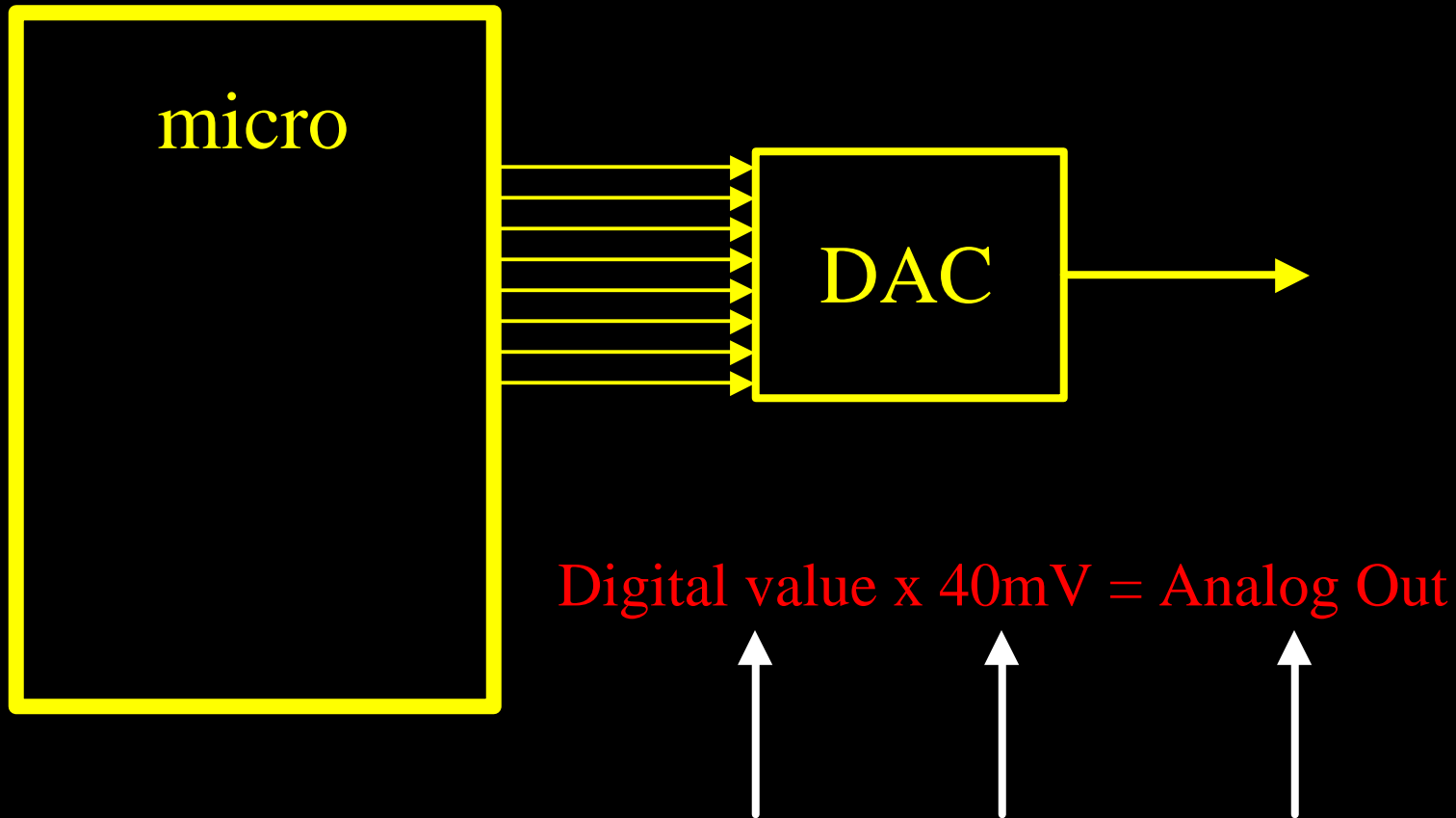


Digital to Analog Converter

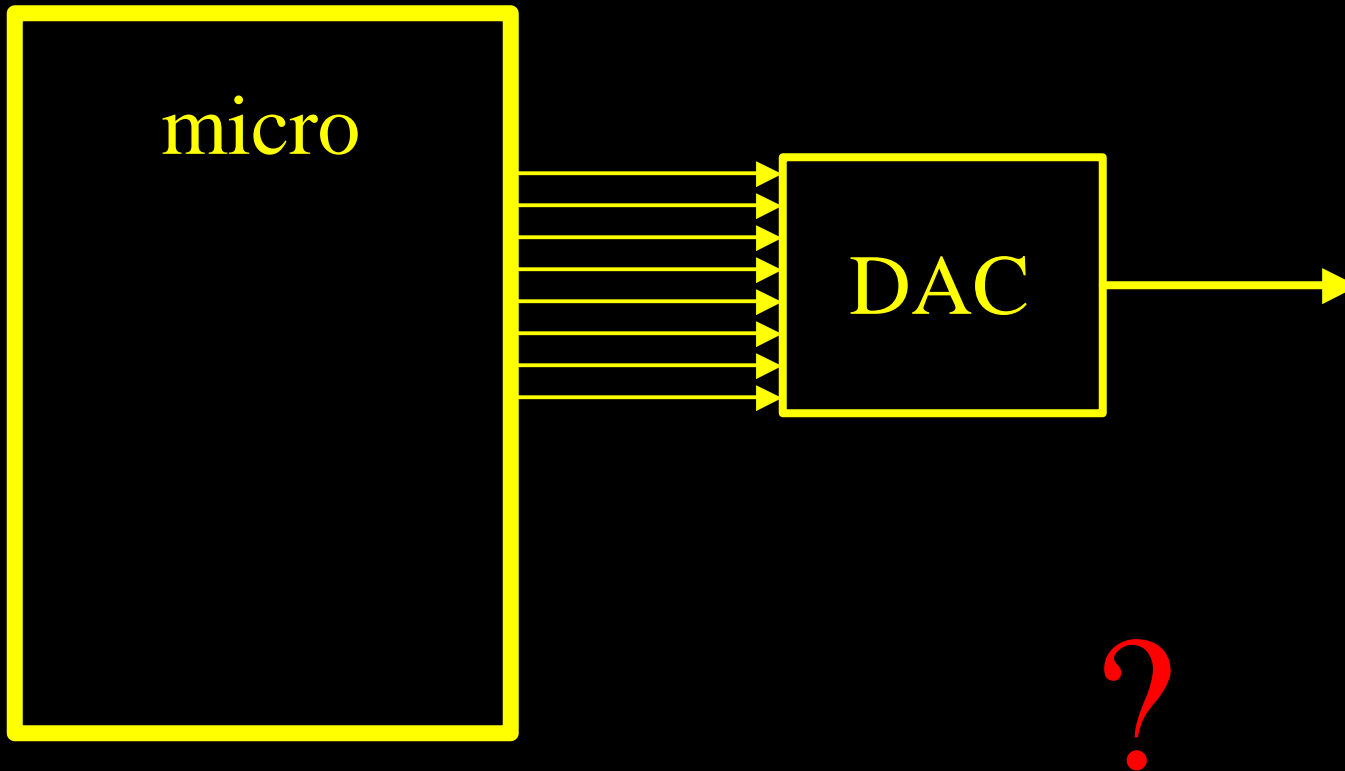


Analog to Digital Converter

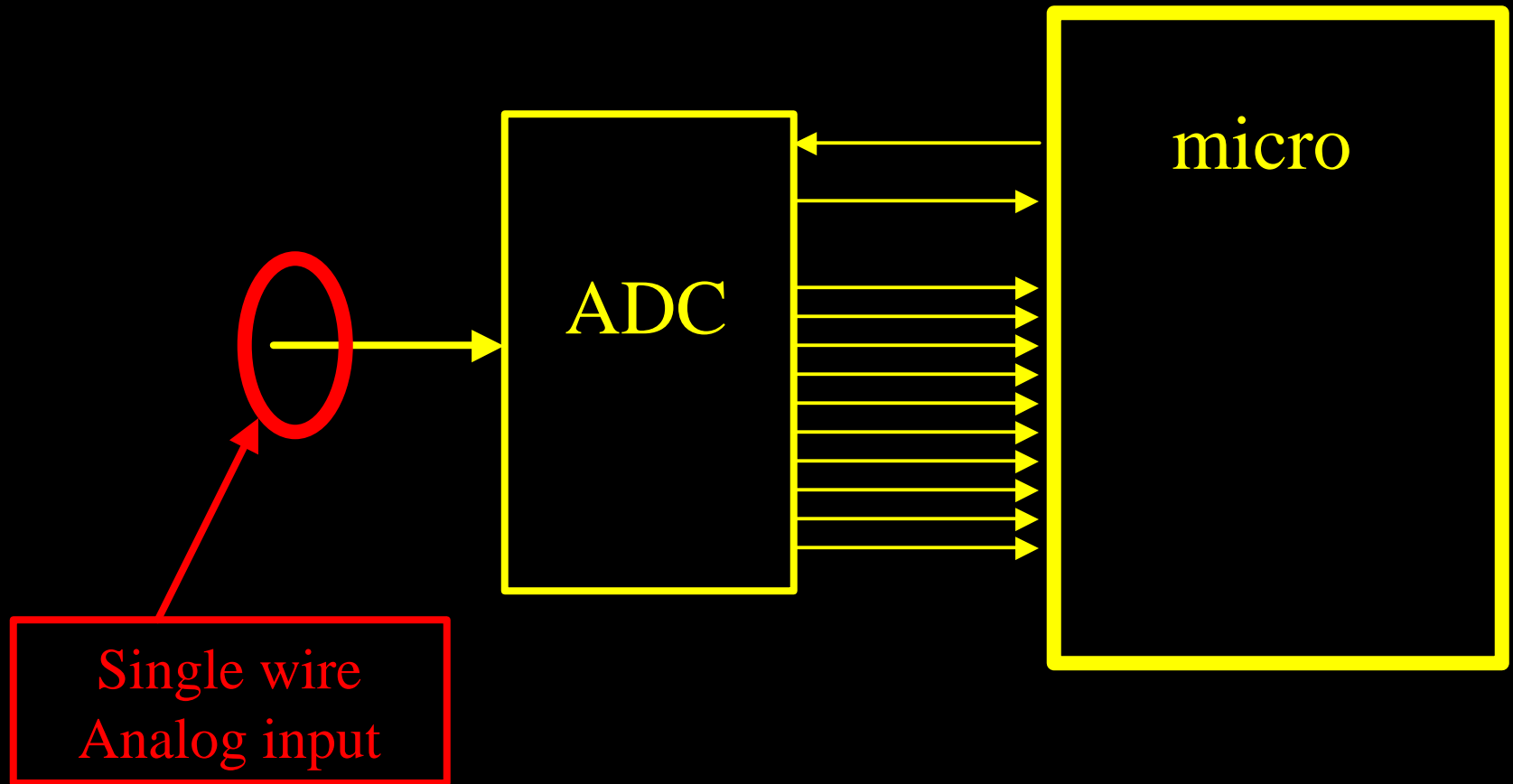


Analog to Digital Converter

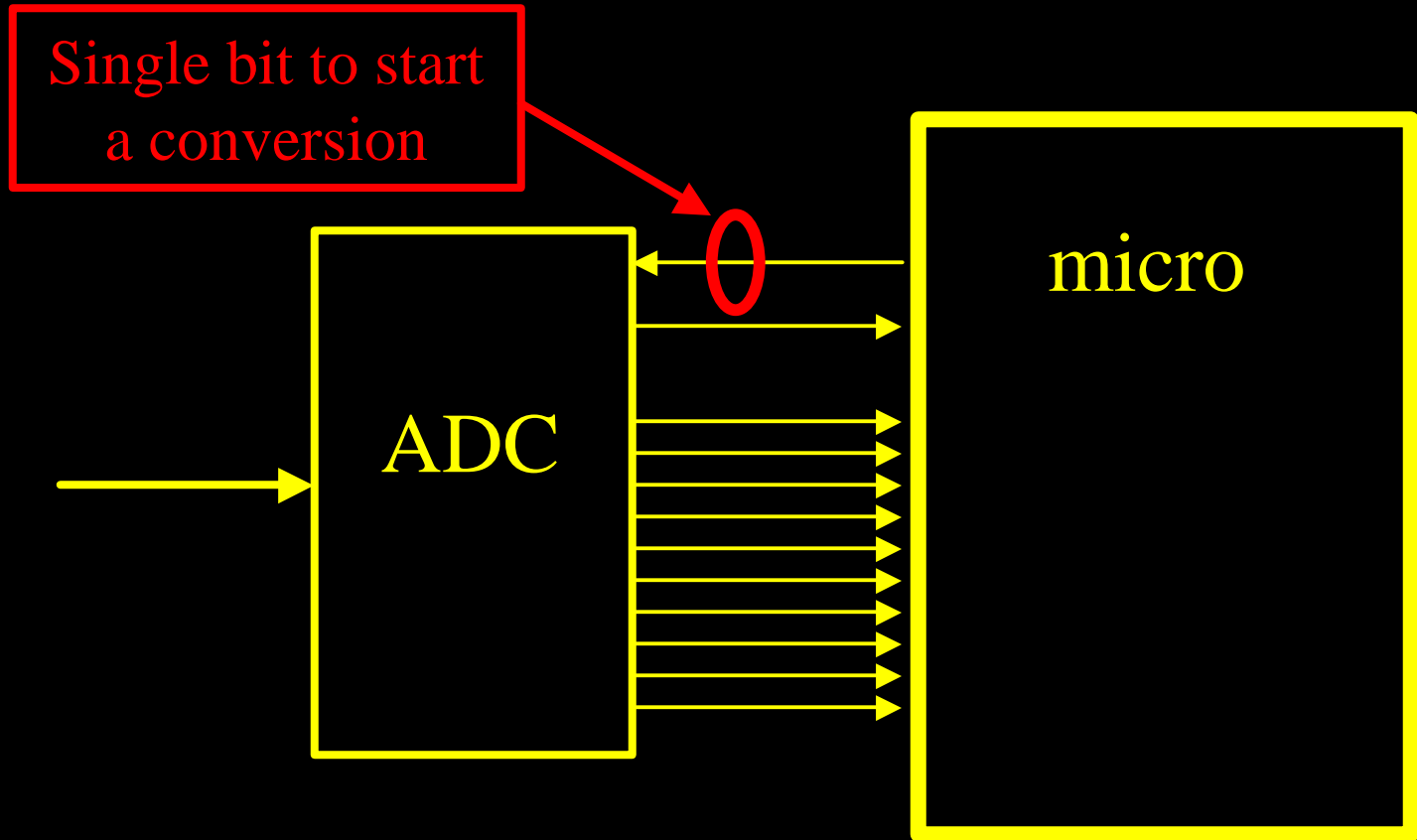


Analog to Digital Converter

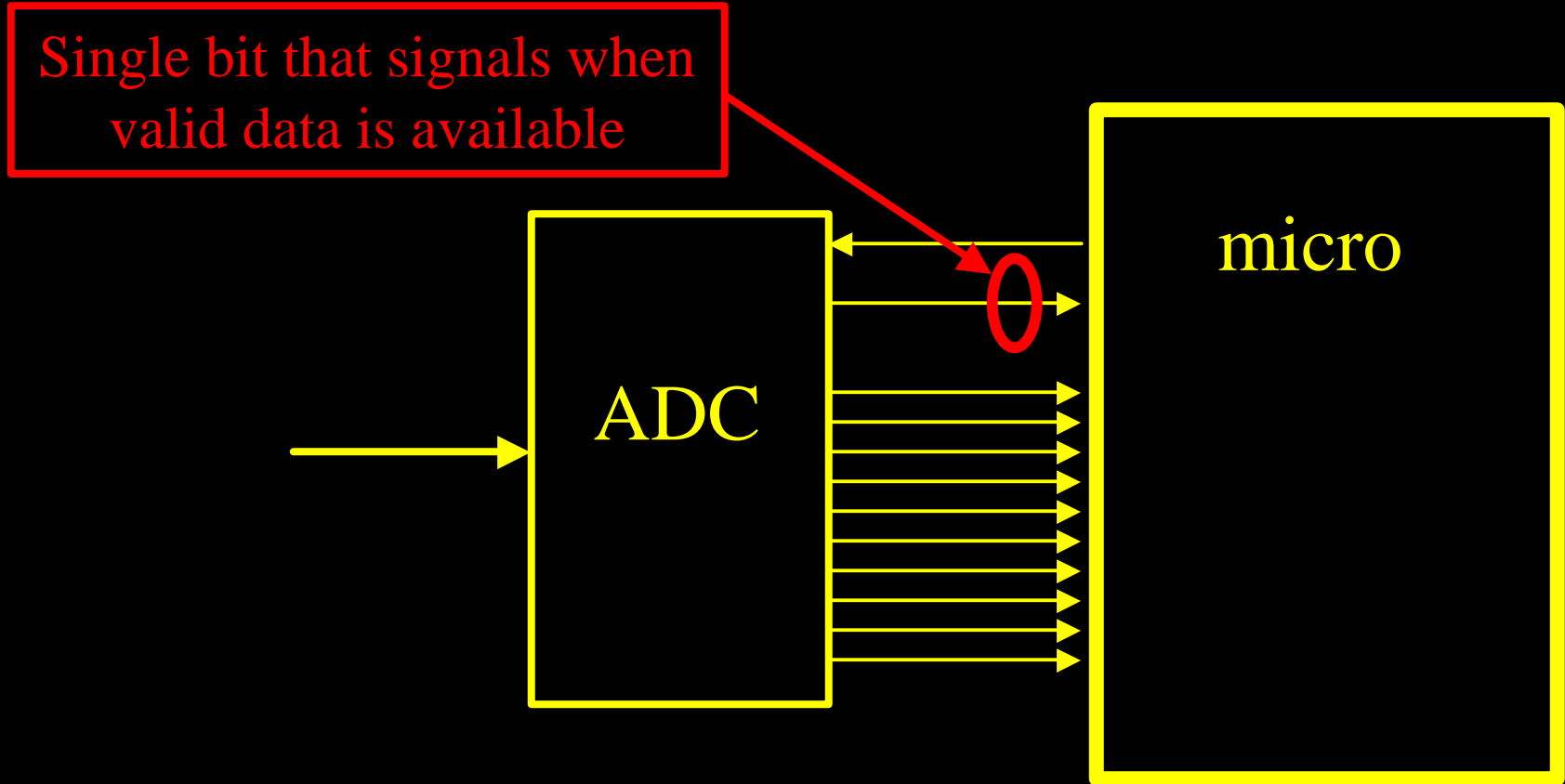

Analog to Digital Converter

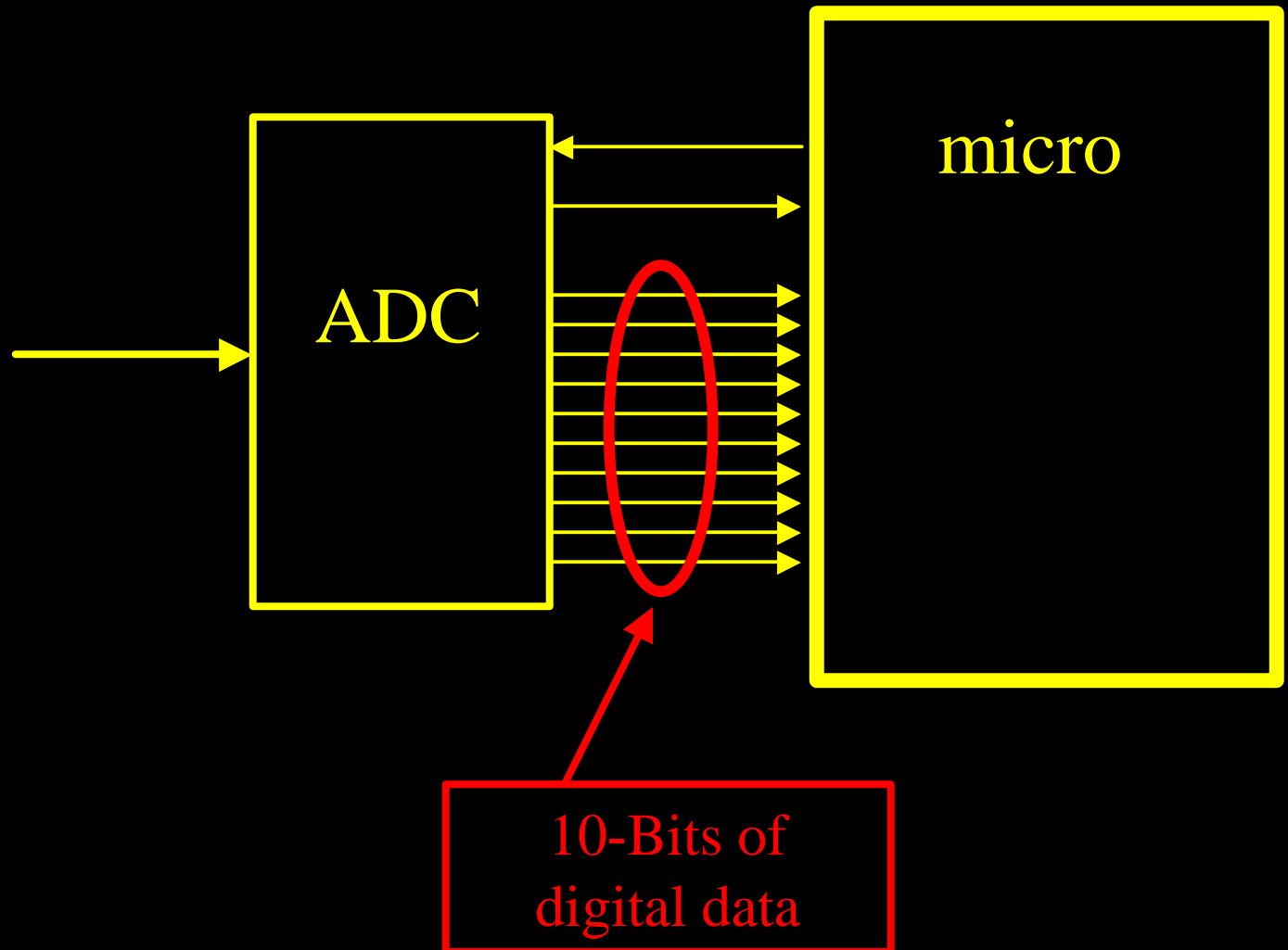


Analog to Digital Converter

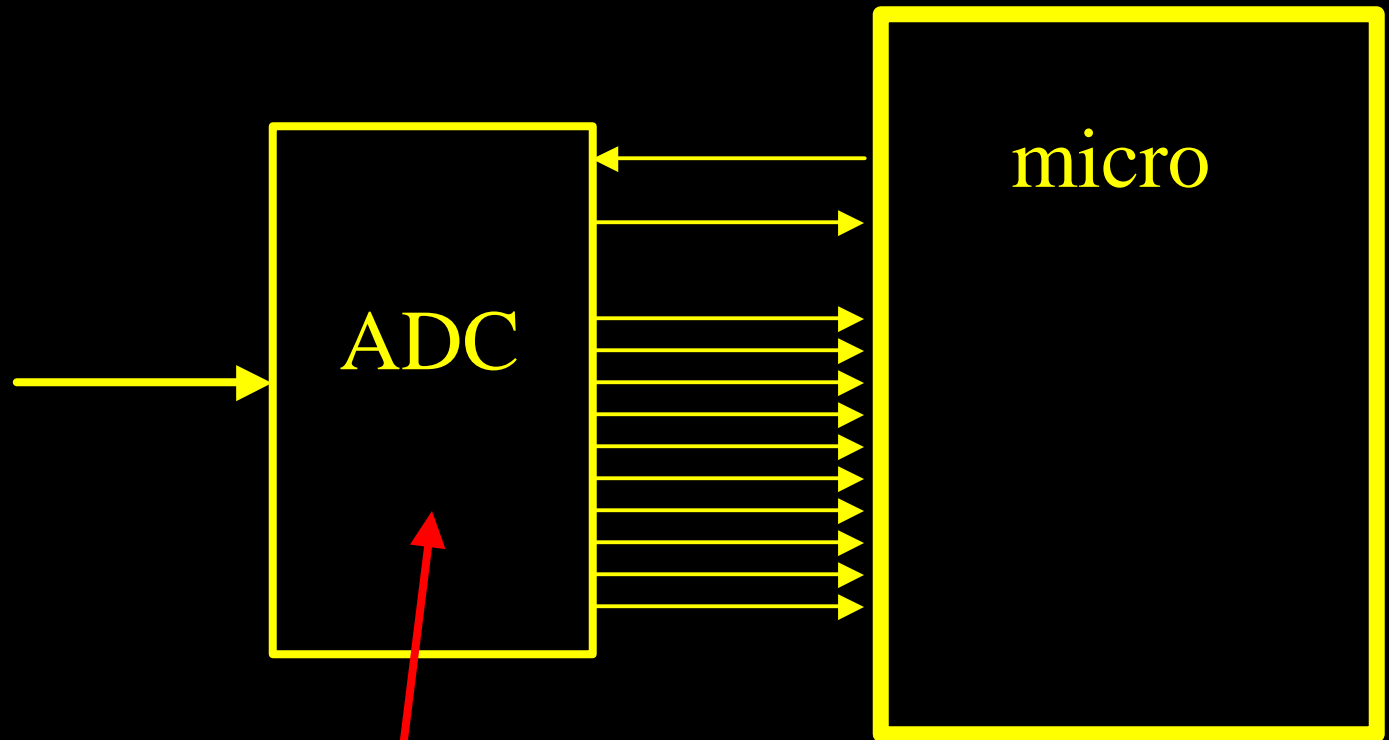


Resolution = 10mV per bit with 10-Bits of data

Analog to Digital Converter

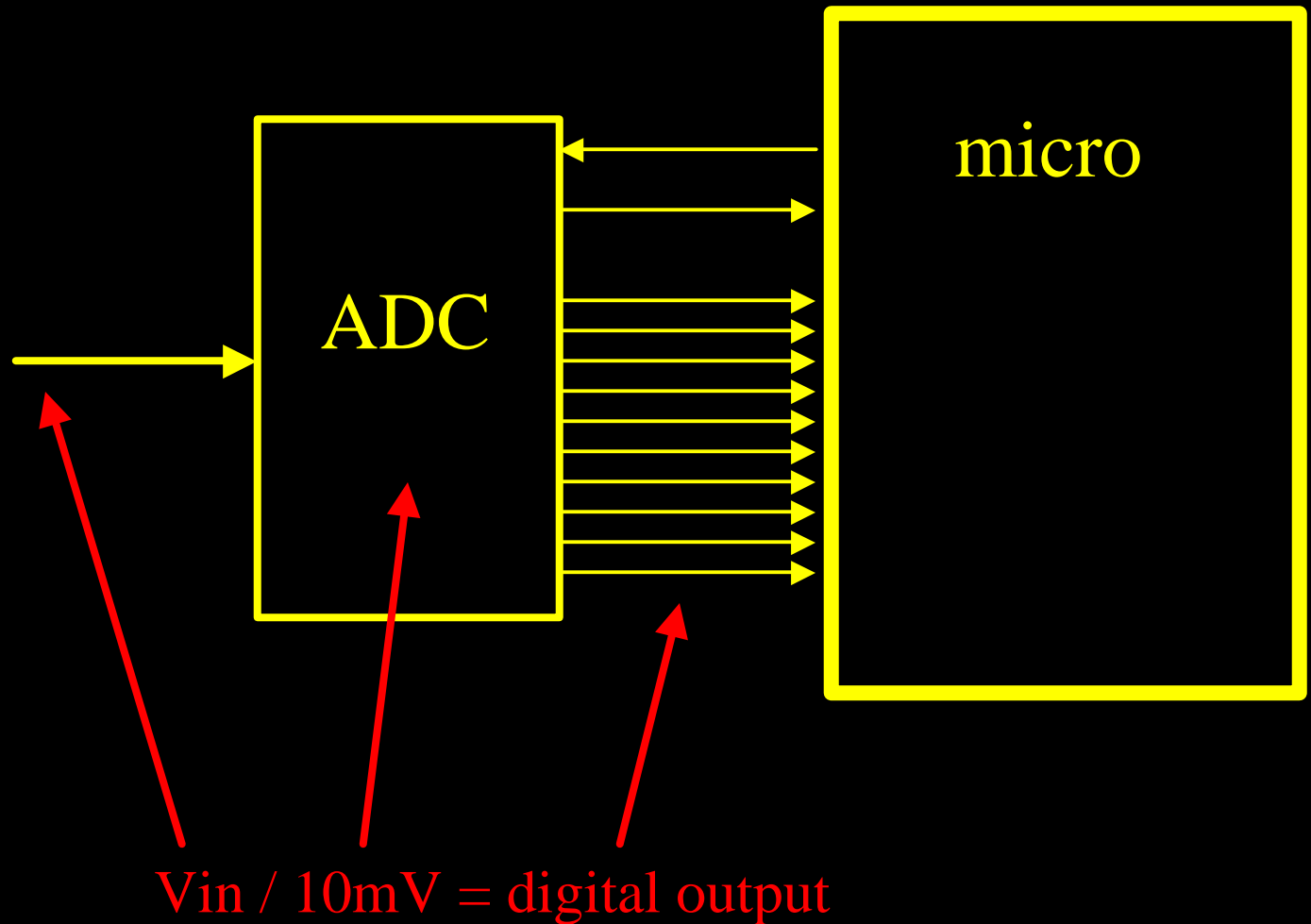


Analog to Digital Converter

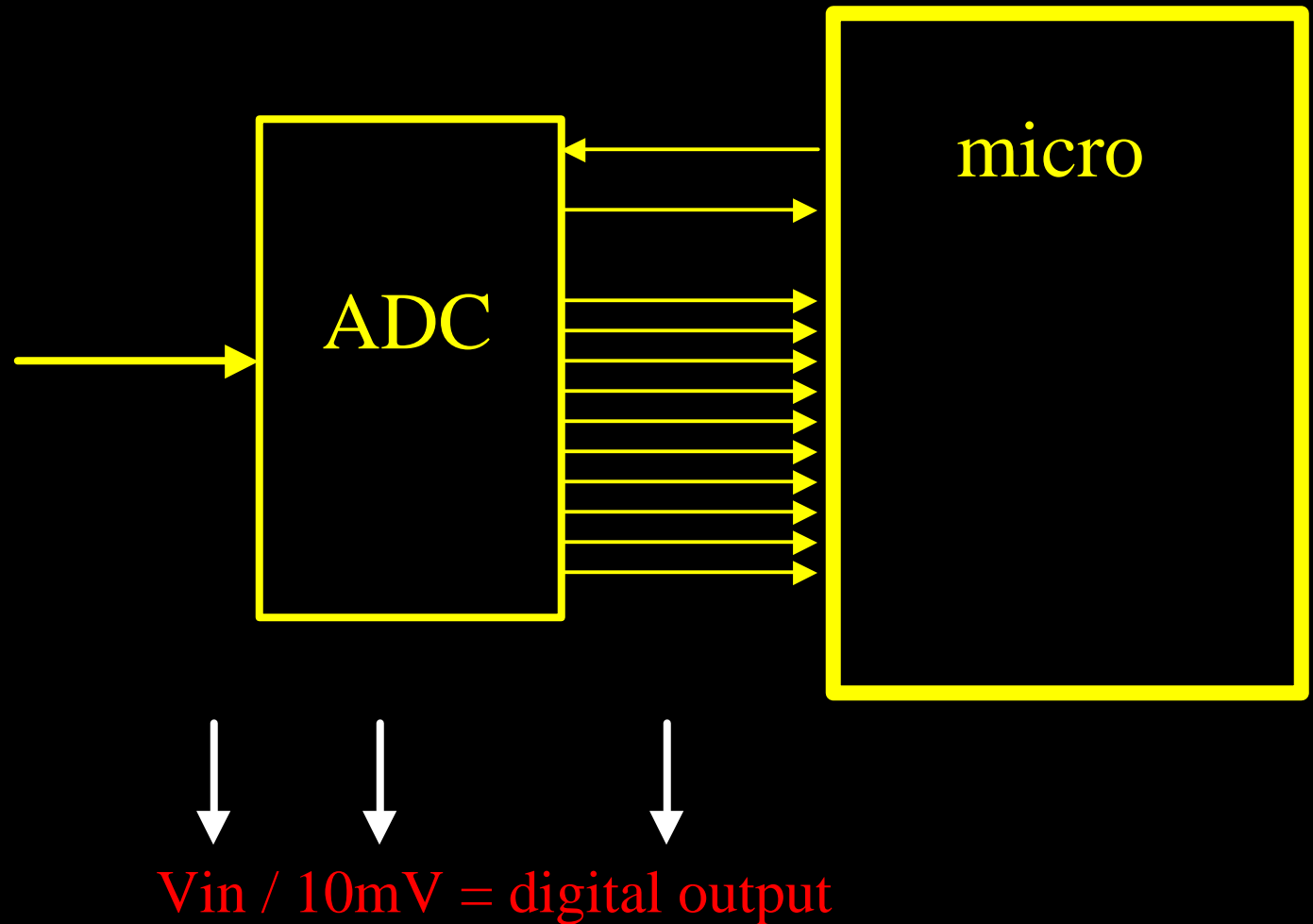


Analog to Digital Converter

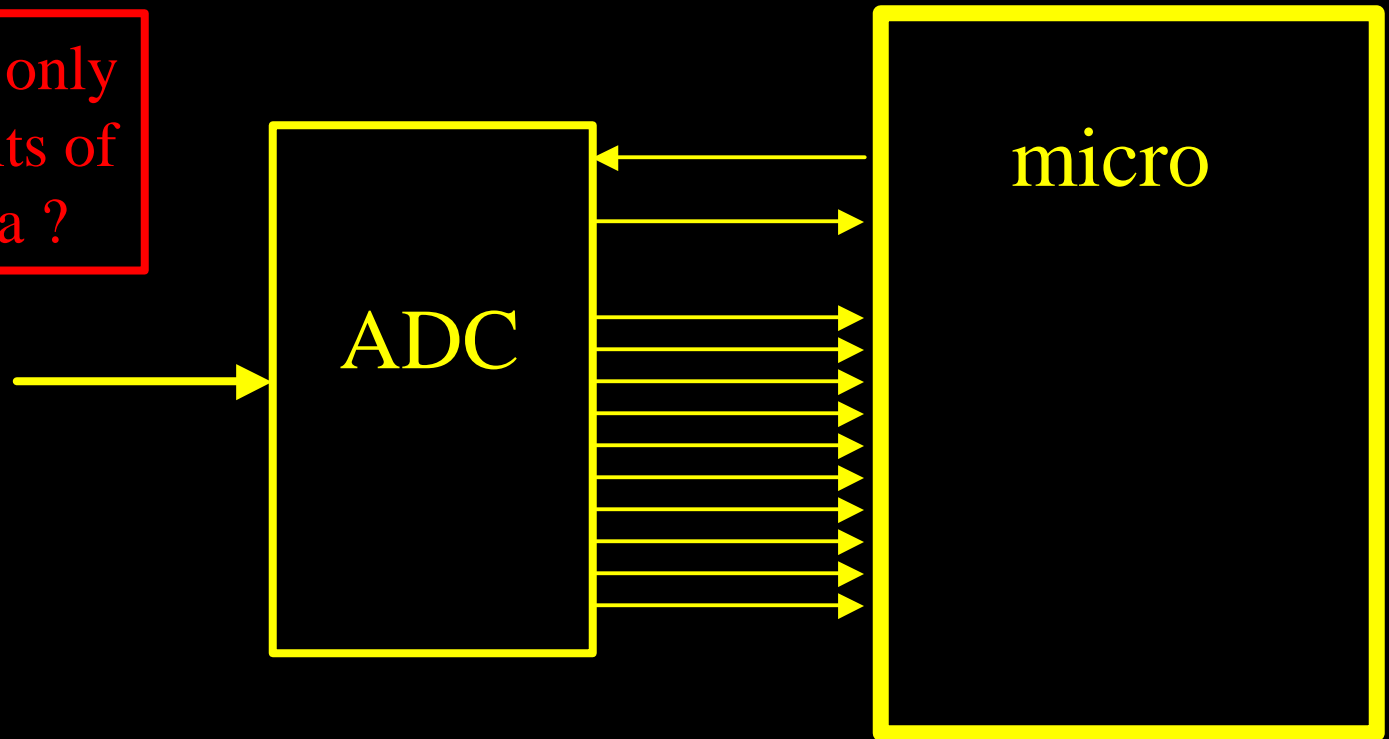
What if, we only
wanted 8-Bits of
digital data ?



Analog to Digital Converter

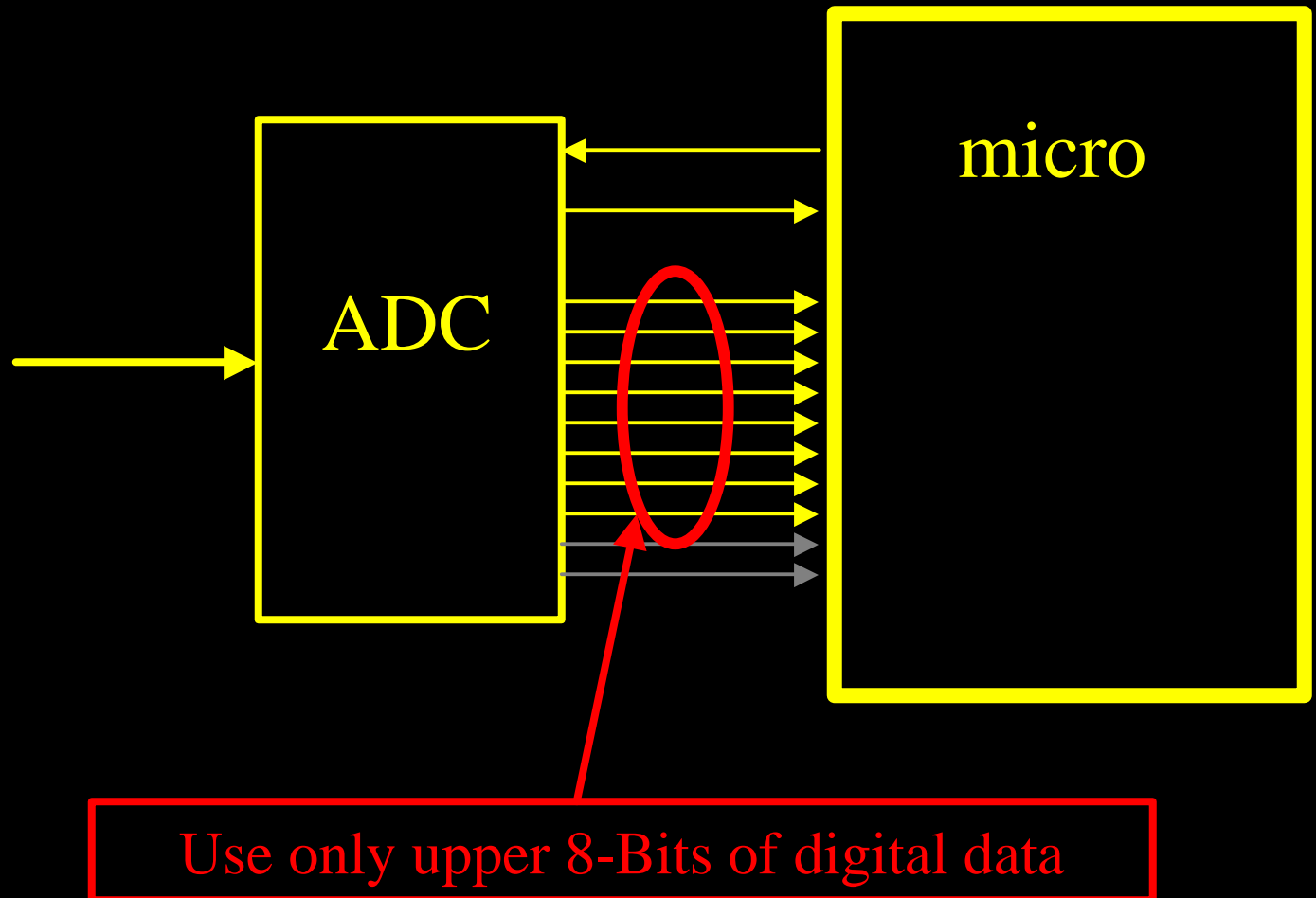


Analog to Digital Converter

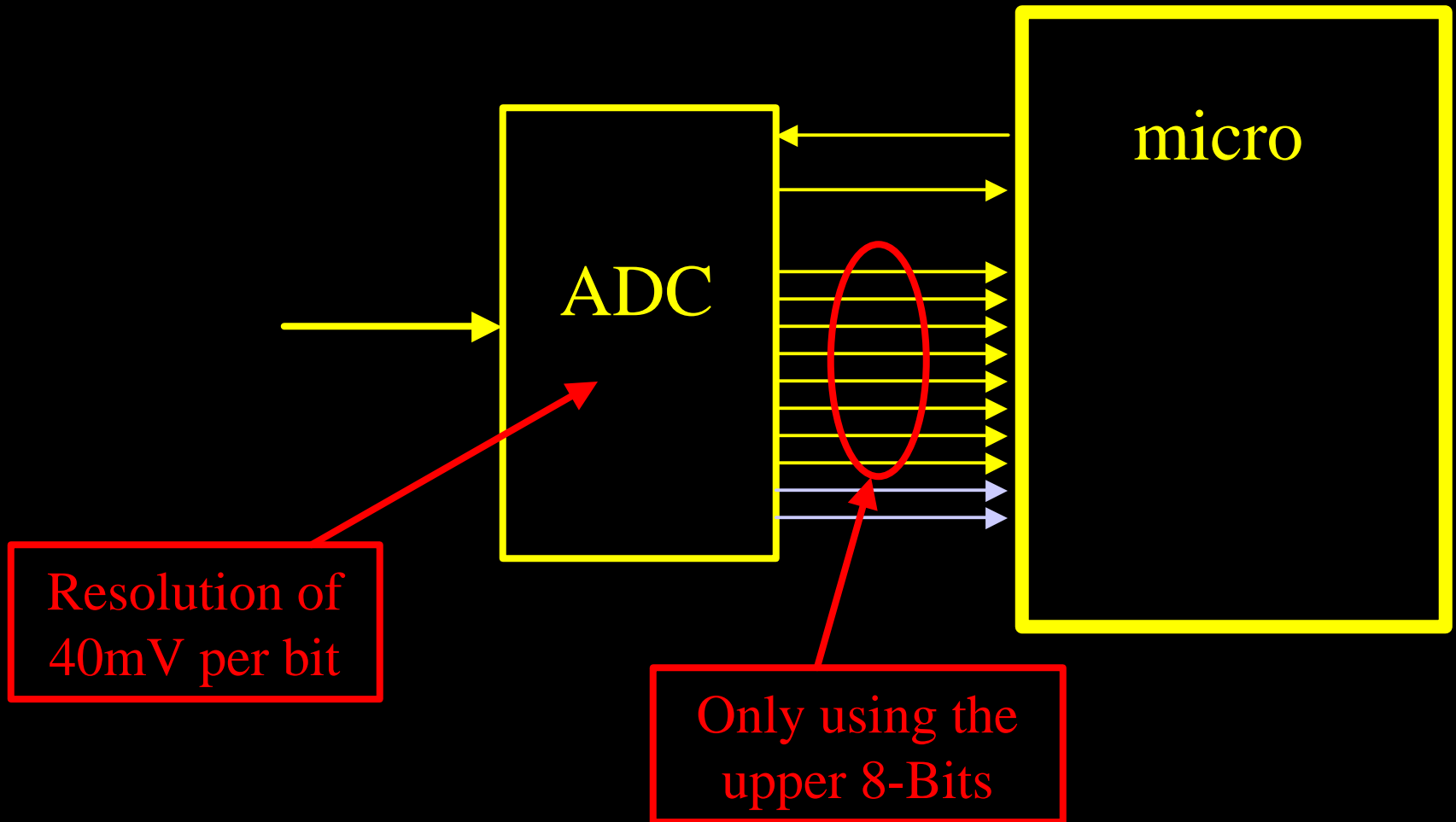

Reading the ADC

Only using the
upper 8-Bits

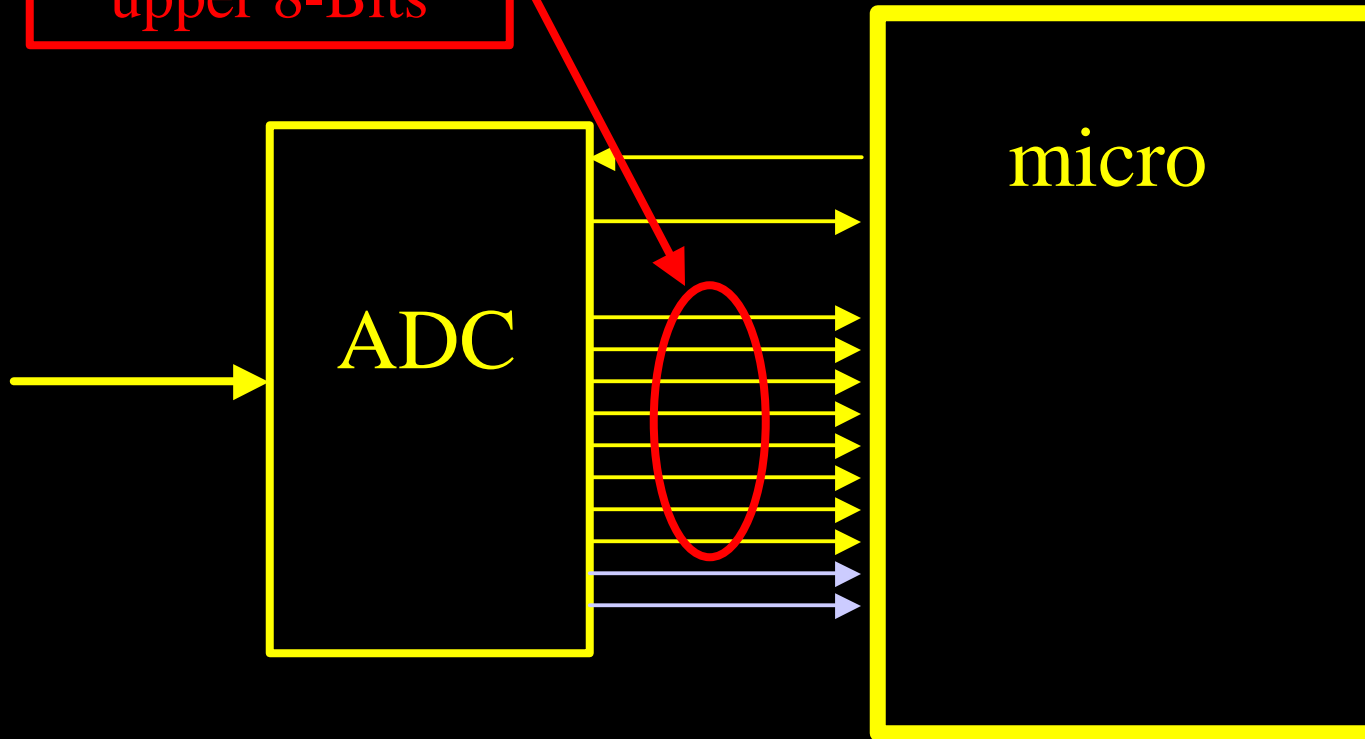


*Assuming
ADC is
connected to
PORTA

analog = PINA;

Reading the ADC

Using all 10-Bits

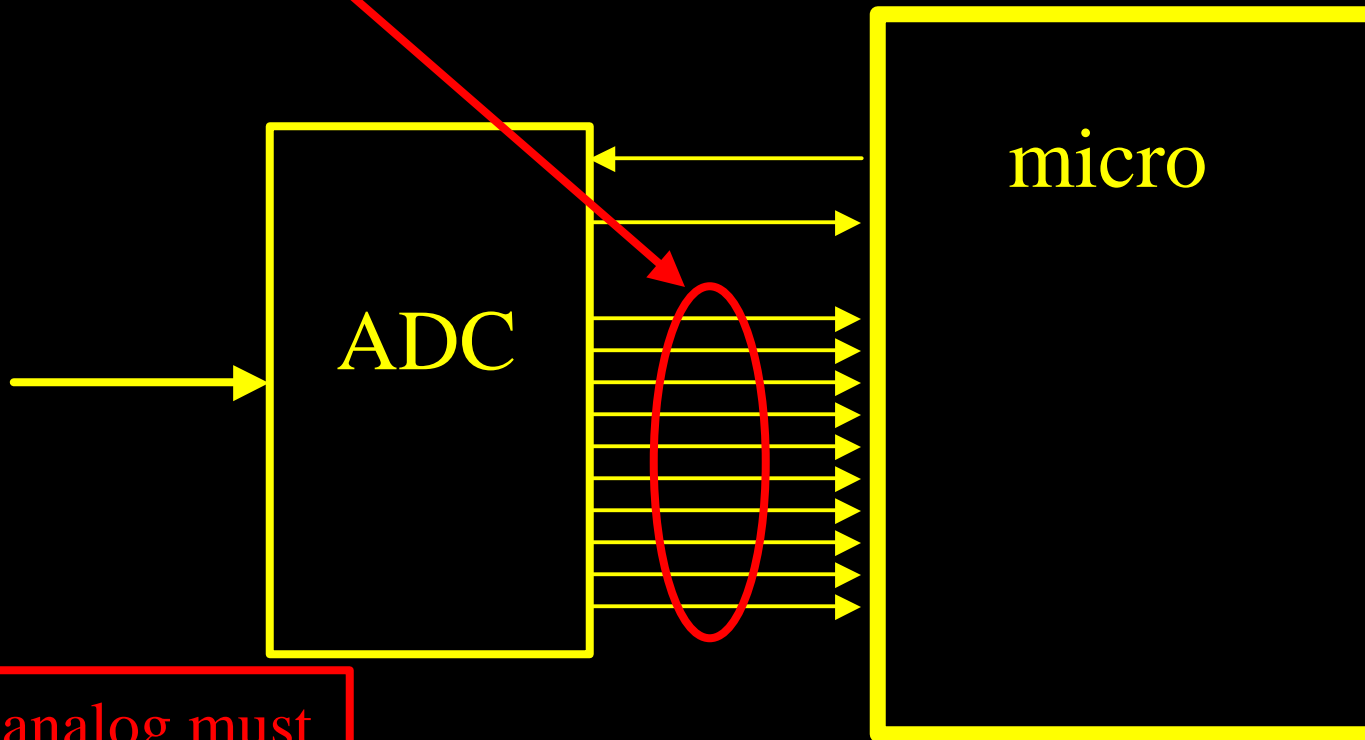


analog must
be an int

```
analog = PINA;  
analog = (analog << 2) | (PINB & 0x03);
```

*Assuming
upper 8-bits
of the ADC
is connected
to PORTA &
the lower 2-
Bits are
connected to
PORTB bits
0 & 1

Reading the ADC

Using all 10-Bits

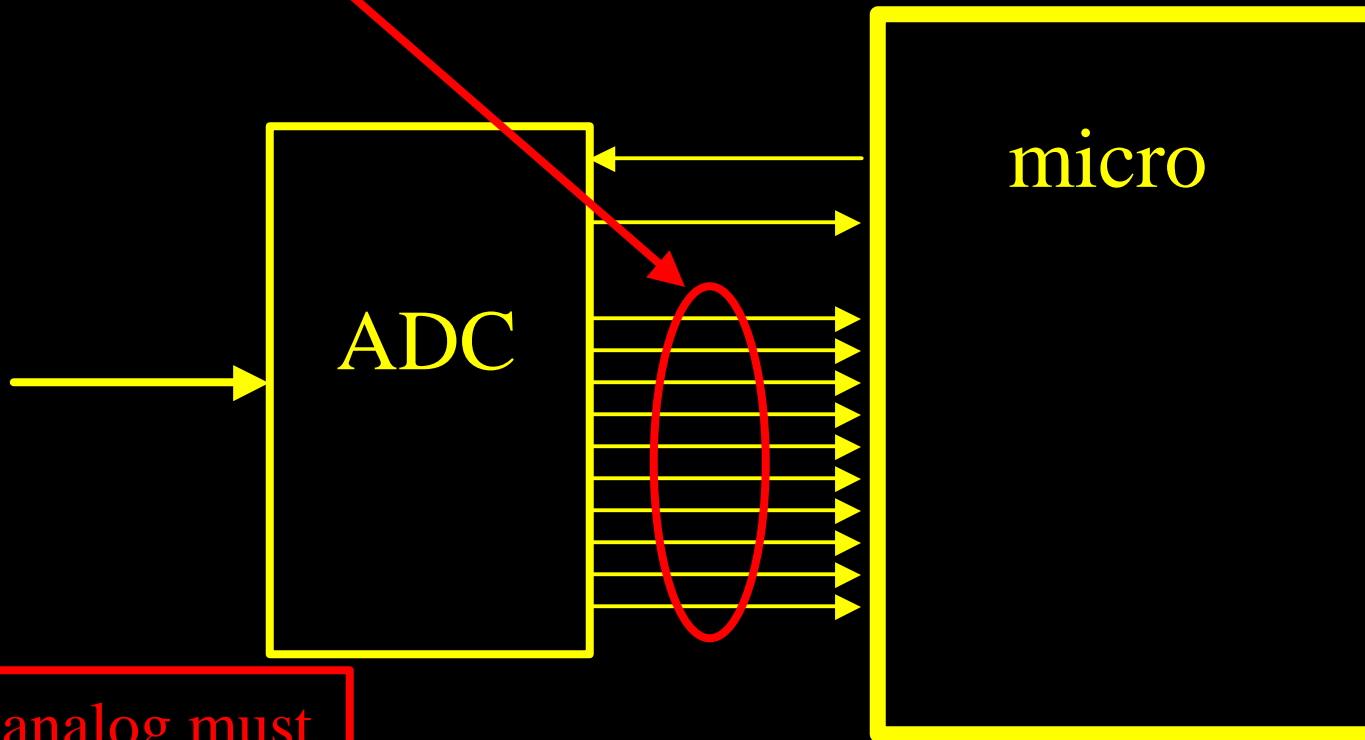


analog must
be an int

```
analog = PINA;  
analog = (analog << 2) | (PINB & 0x03);
```


*Assuming
upper 8-bits
of the ADC
is connected
to PORTA &
the lower 2-
Bits are
connected to
PORTB bits
0 & 1

?

Analog and Digital Converters

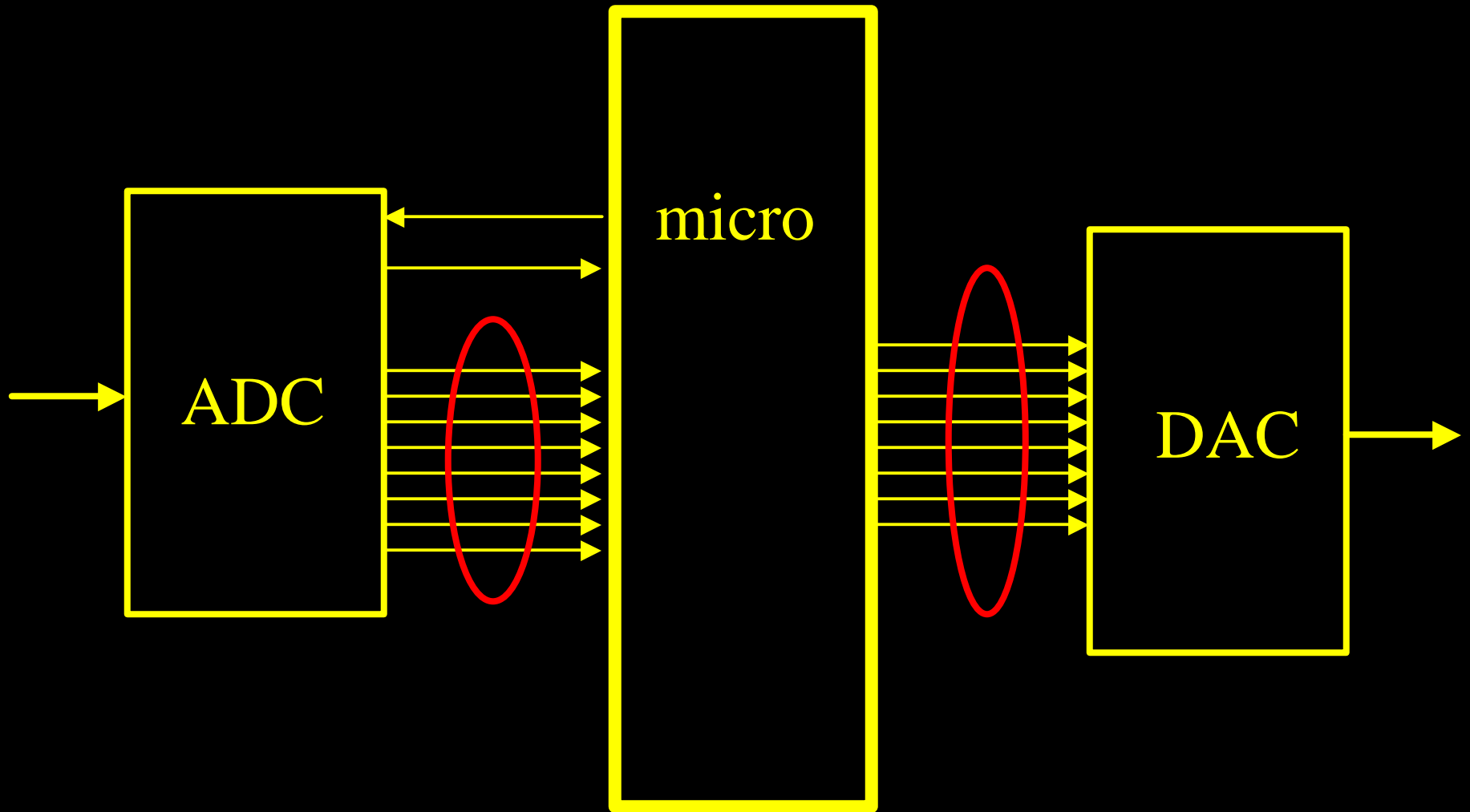


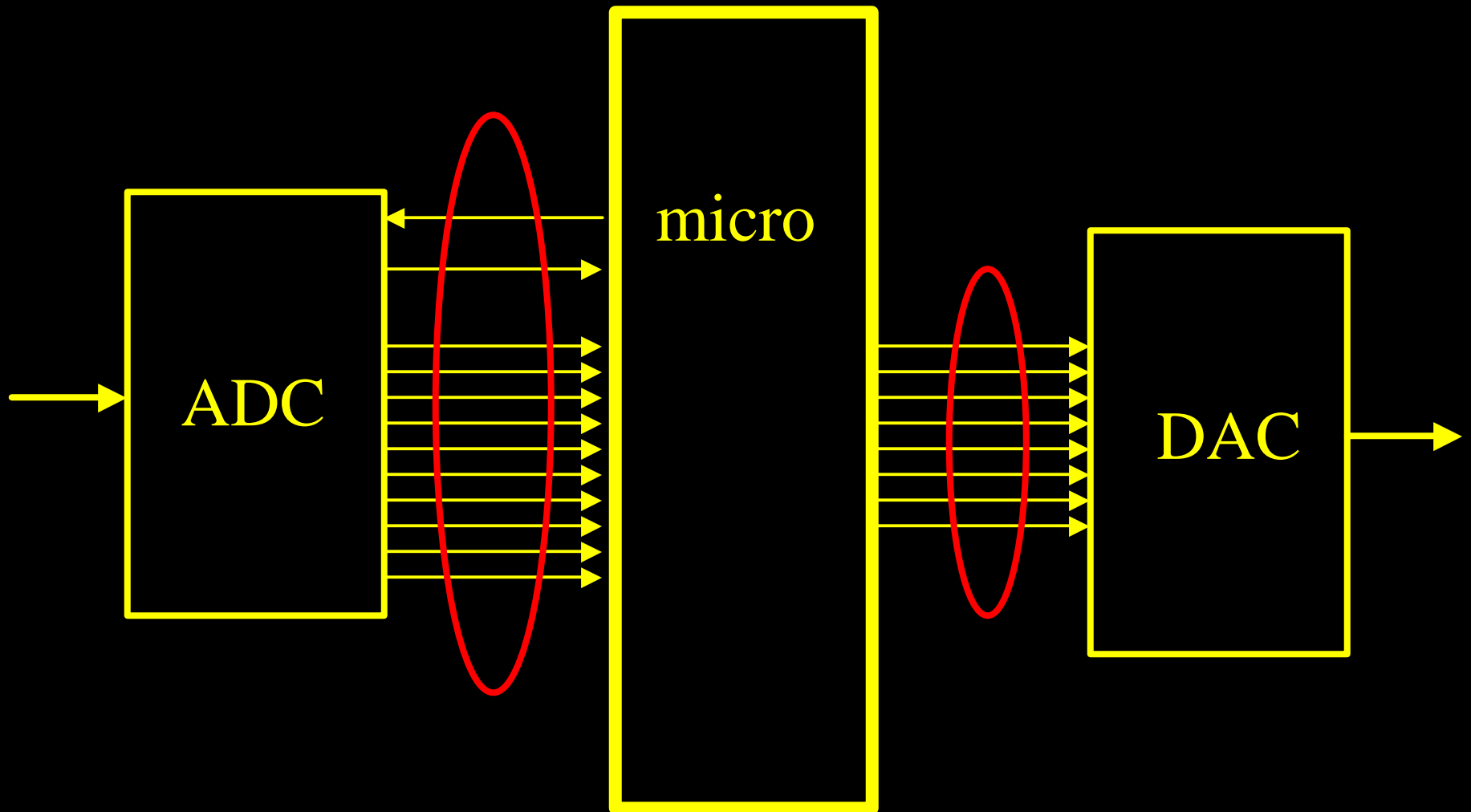Analog and Digital Converter Input and Output Requirements




Analog and Digital Converter

Input and Output Requirements

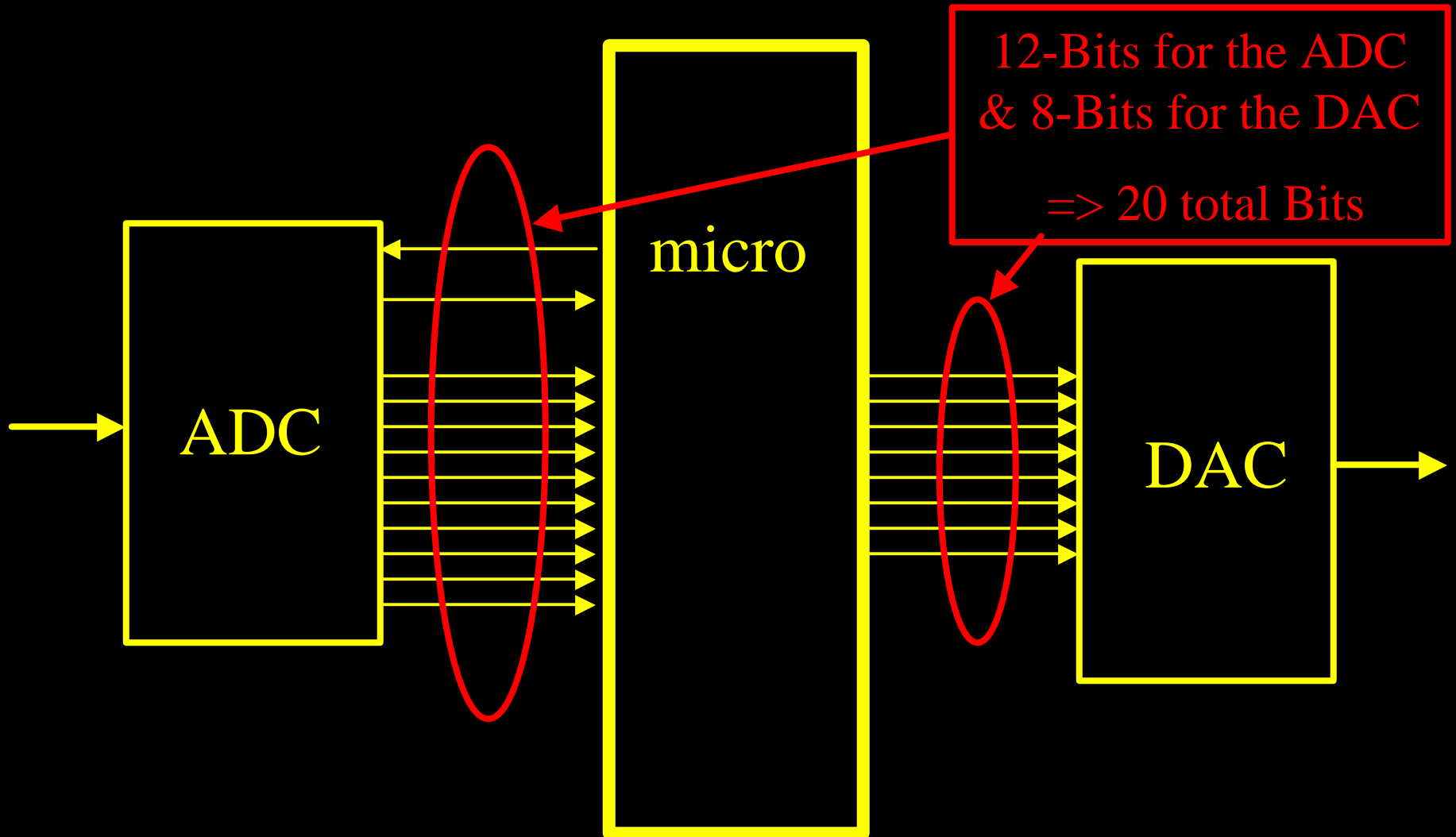

Analog and Digital Converter

Input and Output Requirements

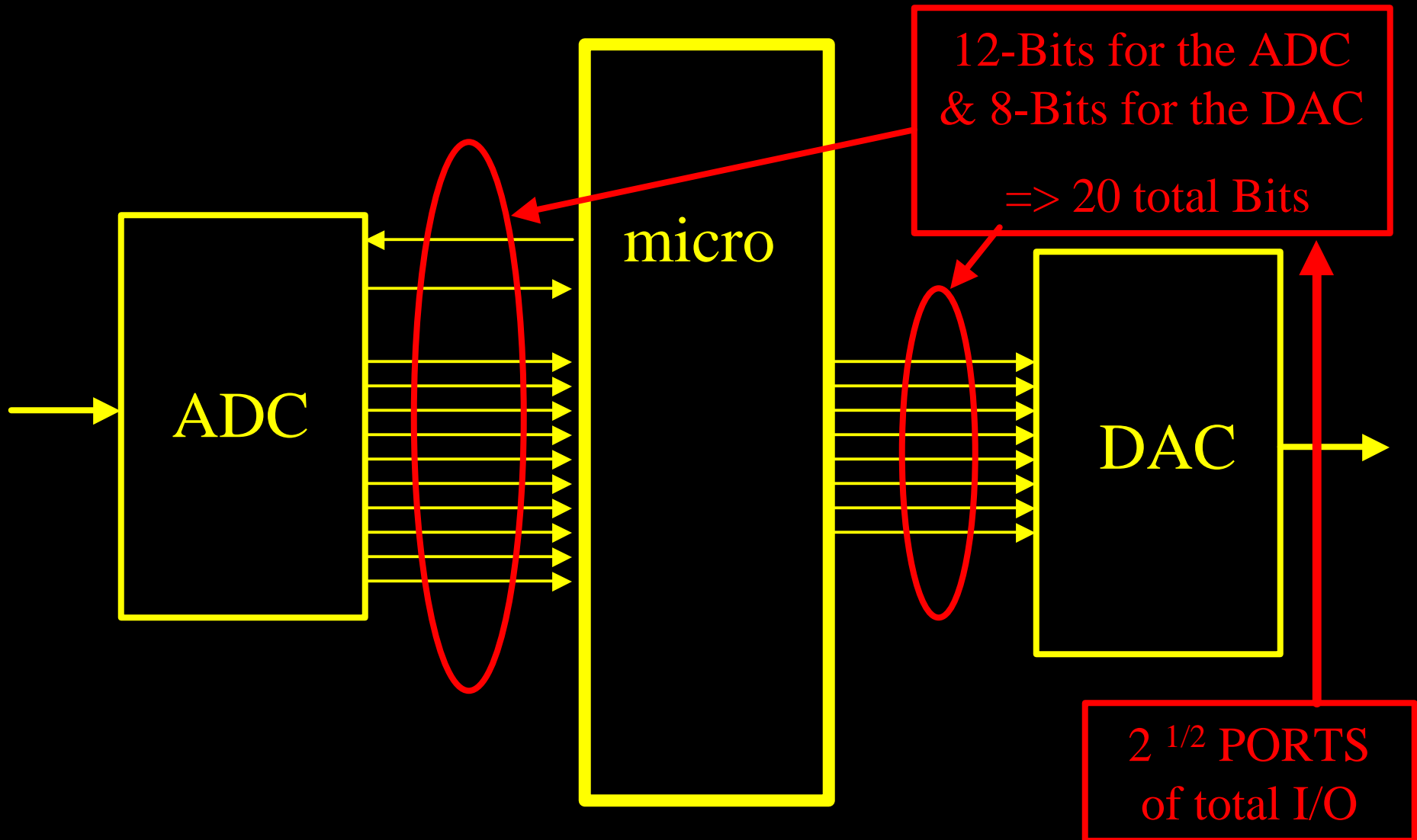


How can we reduce the number
of I/O port pins required?

More on Monday


Lab 9

- Create a Digital Voltmeter!!
- That's pretty straight forward
- Any questions????

Digital Voltmeter

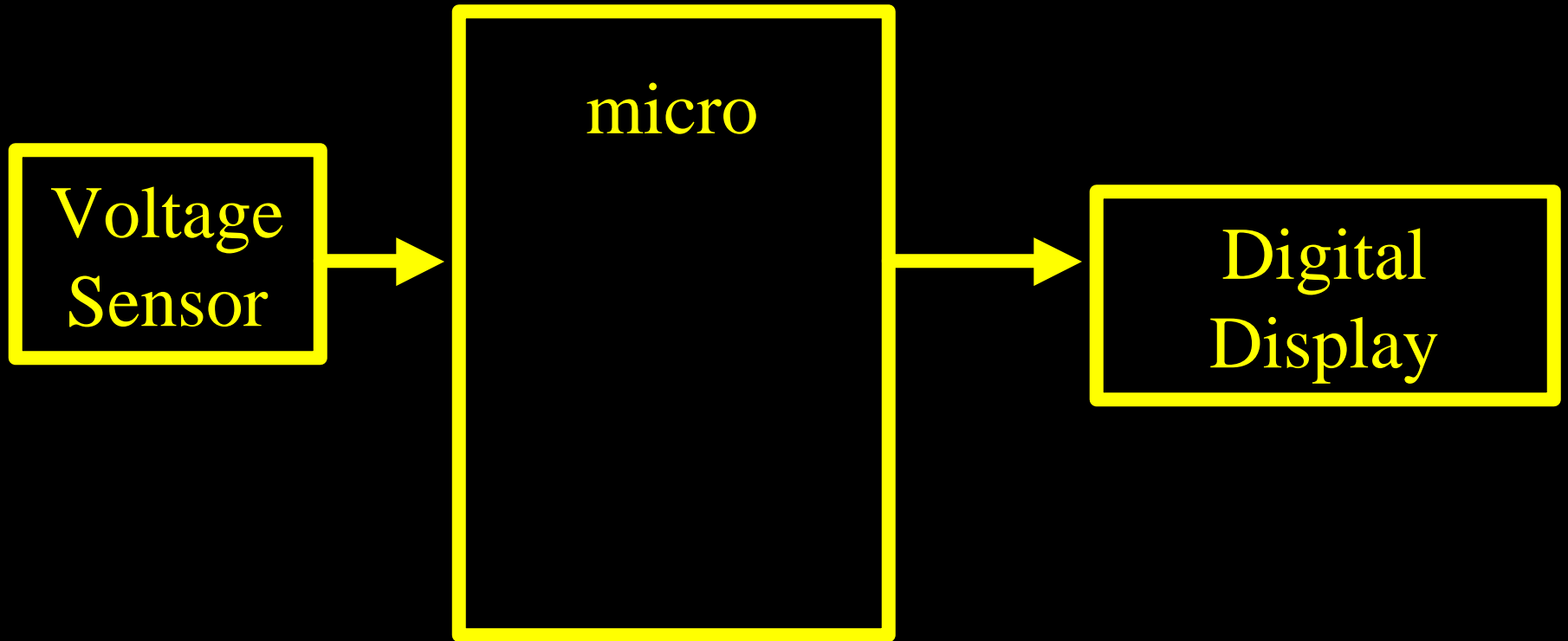

Digital Voltmeter

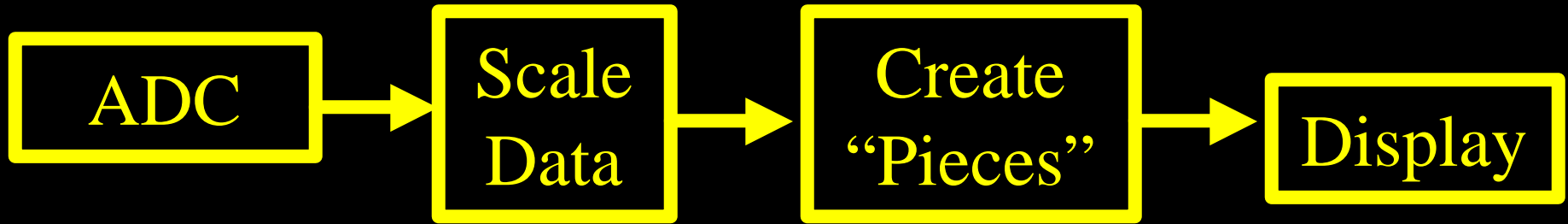

Voltmeter


- Break the project into pieces
 - Read the ADC and print to the terminal
 - Scale the data and print to the terminal
 - Separate the voltage into the BCD components
 - Display the BCD components on the 7-Segs

Solution Steps to use the ADC

1. Set the convert line high
2. Wait for Data Ready to go high
3. Clear the convert line
4. Wait for the Ready Line to go low
5. Read the result of the conversion

Group Activity

Given this ADC I/O Diagram:

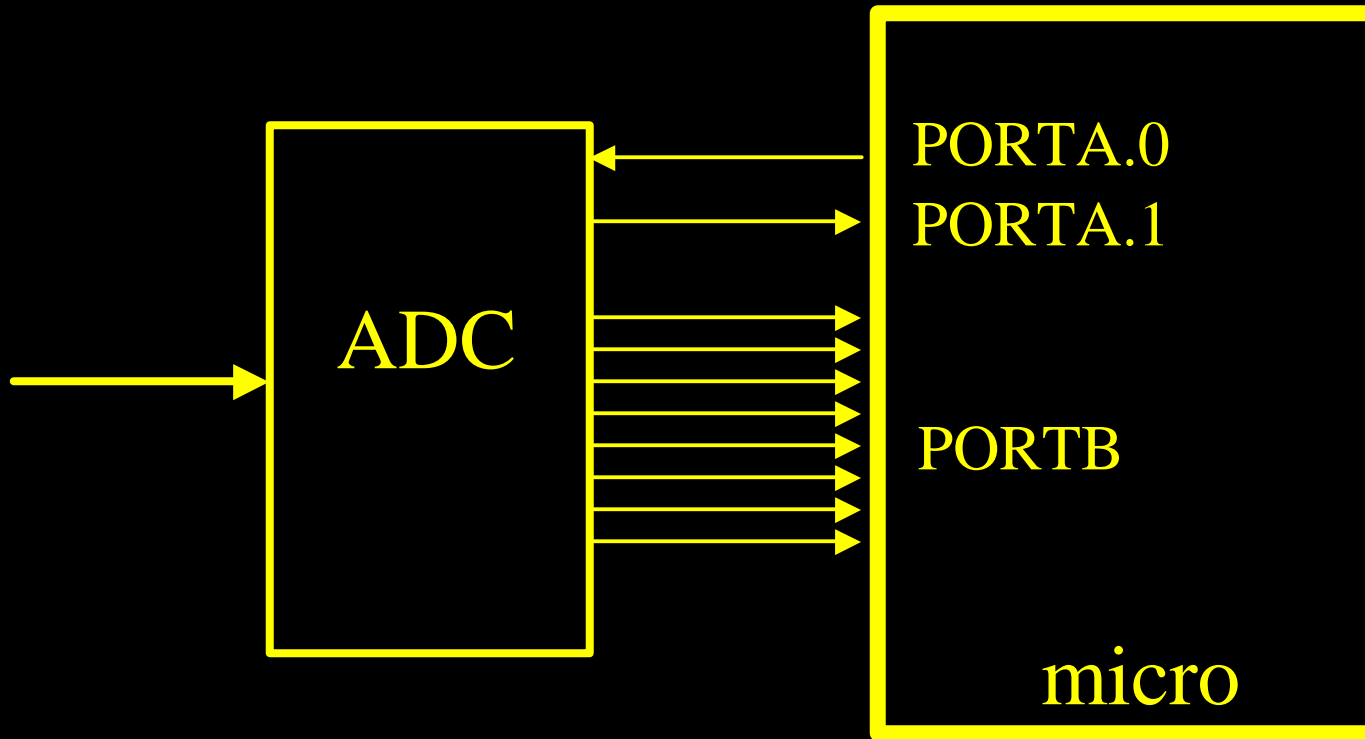

And These Solution Steps

1. Set the convert line high
2. Wait for Data Ready to go high
3. Clear the convert line
4. Wait for the Ready Line to go low
5. Read the result of the conversion

Provide the Following:

- Initialization Code for the I/O Ports
- Draw the software flowchart
- Write the C code to read the ADC

More on Monday